




Control Unit

*Slides modified from Digital IC Design by Pei-yin
Chen and Digital System and Designs and
Practices by Ming-bo Lin and*



Modern Design (1/3)

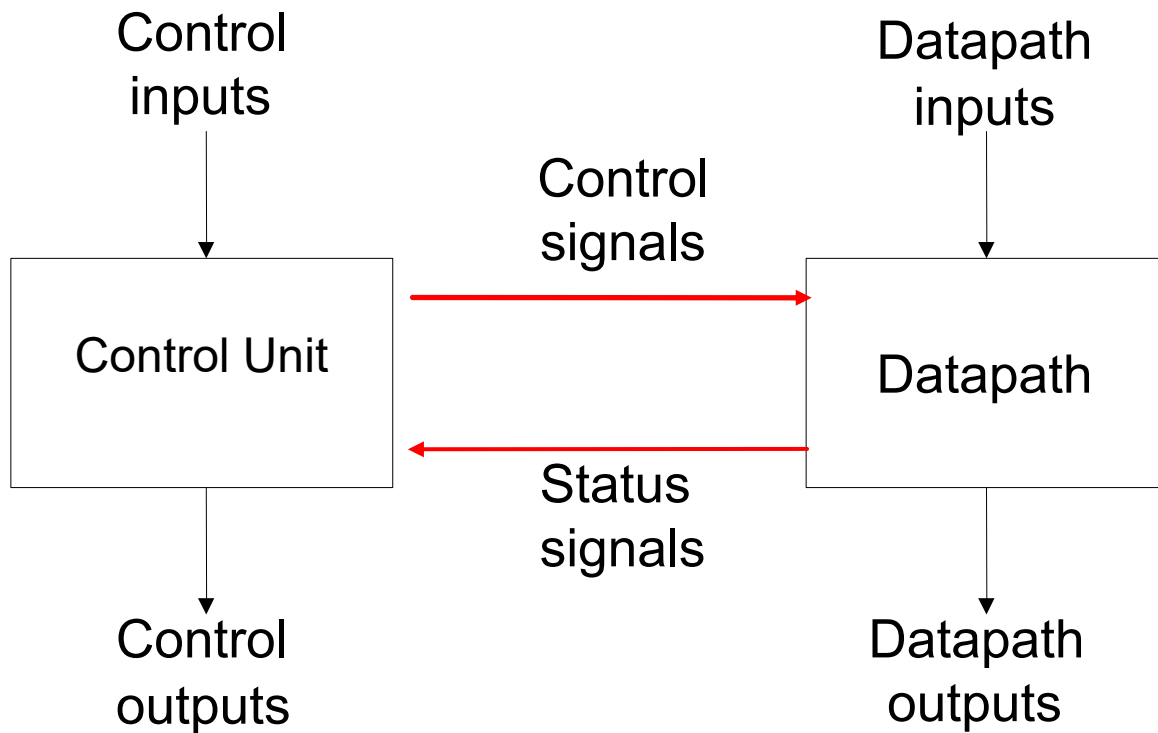Modern design is composed of (1) Datapath and
(2) Controller (control unit or control path)



(Note)


High-level block diagram

Modern Design (2/3)

Register-transfer-level block diagram

C: Combinational circuit

S: Sequential circuit

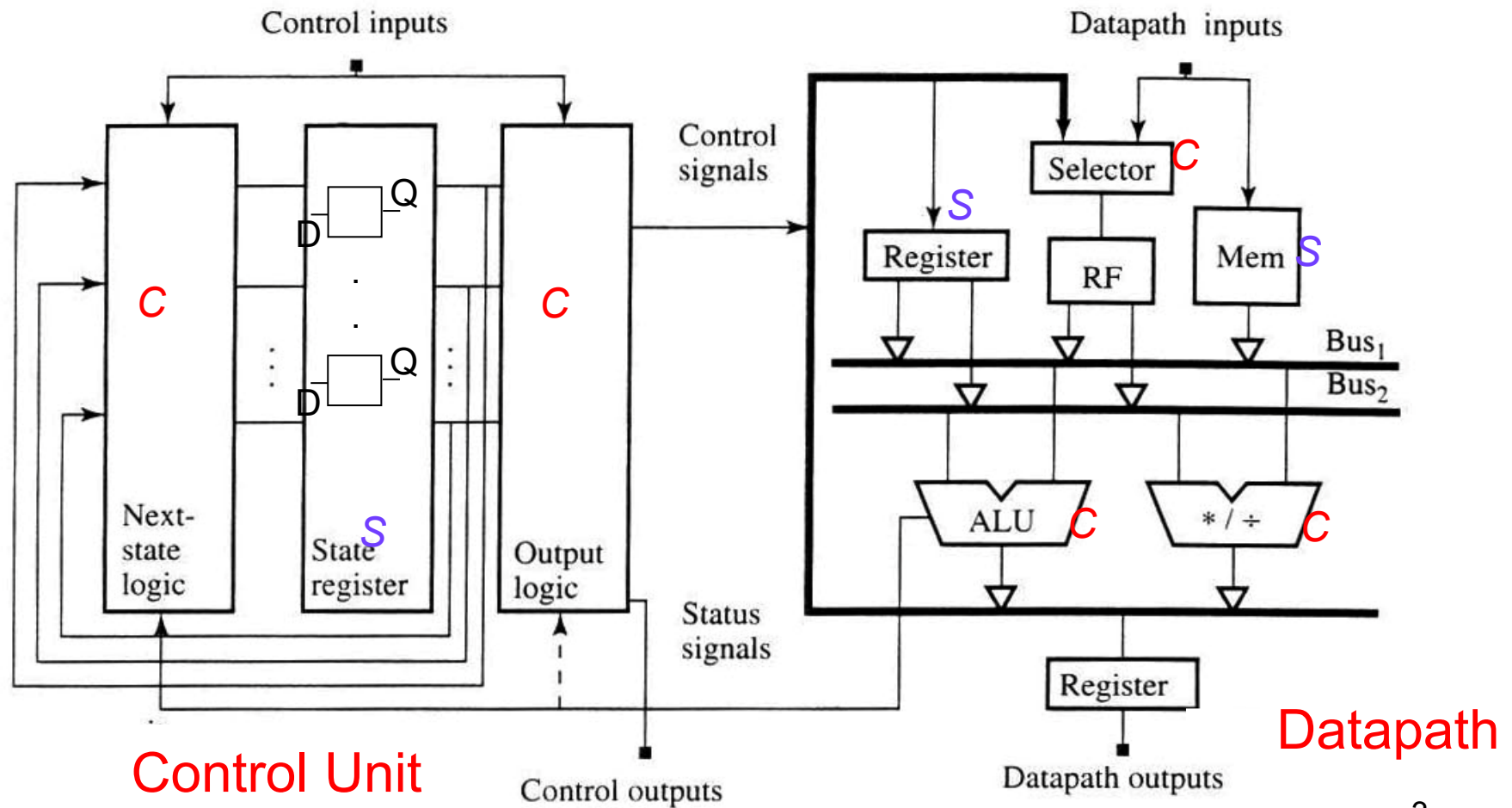


Modern Design (3/3)

How to design
the following →
system??

```
if IR(3) = '0' then
    PC      := PC + 1;
else
    DBUF    := MEM(PC);
    MEM(SP) := PC + 1;
    SP      := SP - 1;
    PC      := DBUF;
end if;
```

SP: Stack Pointer

IR: Instruction Register

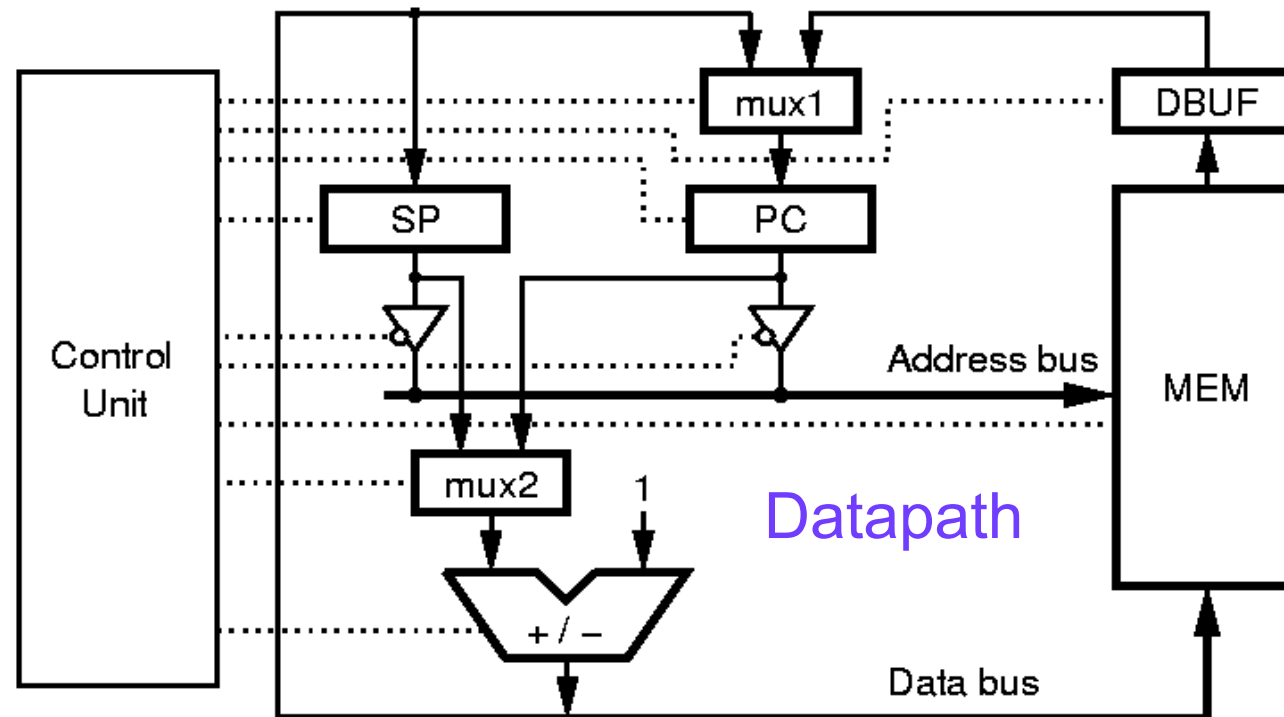


Summation Problem (1/4)

 Question: Calculate $S = x_1 + x_2 + x_3 + x_4 + x_5$ with a ASIC chip

Method 1: Sum up **five** inputs in the same period by using **4** adders

Five inputs must
be ready at
the same time.
Why and How ?



- a. How many input pins and output pins ?
- b. What is the resolutions (bit width) of x_i ?
- c. How fast is the circuit (critical path)?
- d. What is your design cost ?

Summation Problem (2/4)

Calculate $S = x_1 + x_2 + x_3 + x_4 + x_5$

Method_2: Sum up five inputs in the different time units by using only 1 adders

Initial $S = 0$


Time unit _1 $S \leftarrow S + x_1$

Time unit _2 $S \leftarrow S + x_2$

Time unit _3 $S \leftarrow S + x_3$

Time unit _4 $S \leftarrow S + x_4$

Time unit _5 $S \leftarrow S + x_5$

 

Only one input must be ready
at a time. Why?


Cost is lower and **critical path** is **shorter** than the Method_1 .

But its working rate is **slower** than Method_1. (5 clock cycles for 1 summation result)

Summation Problem (3/4)

Problem: Calculate $S = x_1 + x_2 + x_3 + x_4 + \dots + x_{50}$

$$S = \sum_{i=1}^{50} x_i$$

 

If $S_1=0$, $a_1=x_i$

If $S_1=1$, $a_1=y_i$

If $S_2=0, S_3=0$, $r = a_2$

If $S_2=0, S_3=1$, $r = a_1 + a_2$

If $S_2=1, S_3=0$, $r = a_1 - a_2$

If $S_2=1, S_3=1$, $r = a_1$


What is the length of clock period (_____)?

Critical (longest) path delay

⇒ **Reciprocal** is clock rate

Better HDL style

 Separating combinational and sequential circuits



```
module EXAMPLE(data1,data2,clk,q);  
  input  data1, data2, clk;  
  output q;  
  reg    data,q;
```

Combinational
Logic

```
  always @(data1 or data2)  
    data = com(data1,data2);
```

Blocking Assignment

Sequential
Logic

```
  always @(posedge clk)  
    q <= data;  
endmodule
```



Nonblocking Assignment

Design for Summation Problem (1/7)

Method_1

```
module adder1(x1, x2, x3, x4, x5, out);  
input x1, x2, x3, x4, x5;  
output [2:0] out;  
reg [2:0] out;  
  
always@(x1 or x2 or x3 or x4 or x5)  
  
    out=(((x1+x2)+x3)+x4)+x5;  
  
endmodule
```

  Calculate $S = x_1 + x_2 + x_3 + x_4 + x_5$





Design for Summation Problem (2/7)

Method_2 (shorter delay)

```
module adder2(x1, x2, x3, x4, x5, out);  
input x1, x2, x3, x4, x5;  
output [2:0] out;  
reg [2:0] out;
```
  
```
always@(x1 or x2 or x3 or x4 or x5)  
    out=((x1+x2)+(x3+x4))+x5;  
endmodule
```



Unstable output (Delay is 3*kns -- less than Method_1)

Design for Summation Problem (3/7)



Method_3 (Using registered output)

```
module adder3(x1, x2, x3, x4, x5, clk, out);  
input x1, x2, x3, x4, x5, clk;  
output [2:0] out;  
reg [2:0] out;
```

```
always@(posedge clk)
```

```
out=((x1+x2)+(x3+x4))+x5;
```

```
endmodule
```

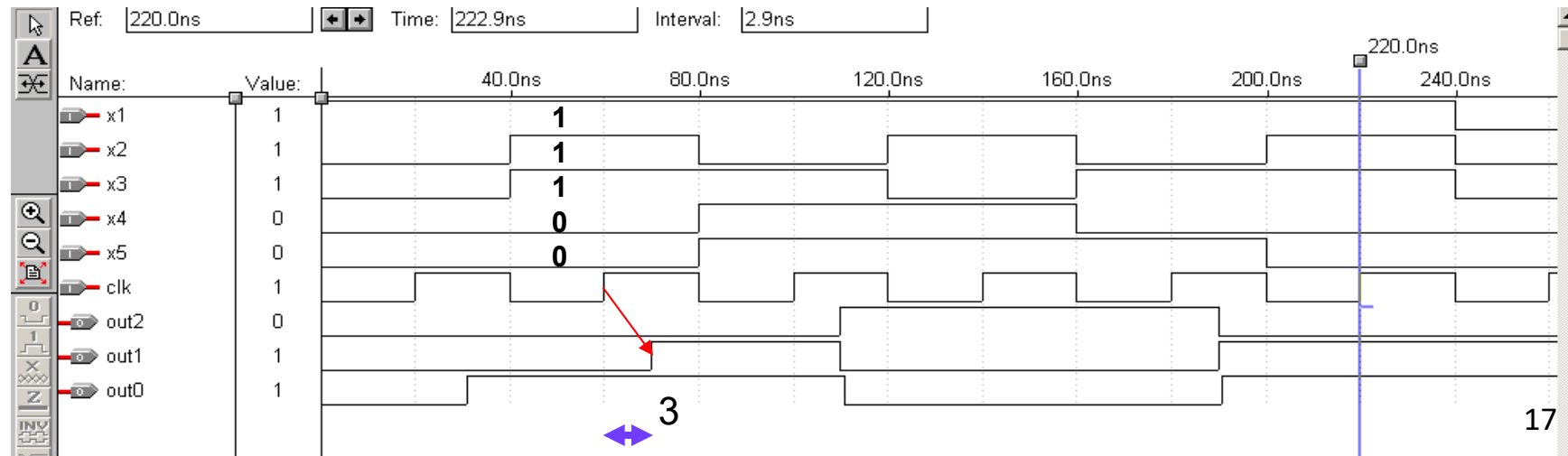 


Stable output with register (3-bit flip-flop) Delay is 3*kns+cns (reg assign delay)

Design for Summation Problem (4/7)

Method_4: Using pipelined register

 
```
module adder4(clk, x1, x2, x3, x4,  
x5, out);  
input clk,x1, x2, x3, x4, x5;  
output [2:0] out;  
reg [2:0] out, temp1, temp2,temp3;  
always@(posedge clk)  
begin  
    temp1<=(x1+x2)+x3;  
    temp2<=x4;    temp3<=x5;  
    out<=temp1+temp2+temp3;  
end  
endmodule
```



Delay is $2*kns+cns$, which is less than Method_1 (4kns), Method_2 (3kns) and Method_3 (3kns+cns)

So, this method can achieve the best (fastest) clock rate because its critical path is shortest. However, the correct **out** is generated after **two clock cycles** not just one (also named as datapath pipelining)

Design for Summation Problem (5/7)

 


- 1. Wire delay
- 2. Register assignment delay

Critical path is about 4kns

A correct output is generated every clock cycle

Event	1	2	3	4	5	6
Completed time	4k	8k	12k	16k	20k	24k

 


Critical path is about 2.5 kns, why? faster clock rate

A correct output is generated after two clock cycles


Event	1	2	3	4	5	6
Completed time	5k	7.5k	10k	12.5k	15k	17.5k

Two events are parallel processed in the unit.
Faster clock rate but higher cost (3 extra regs)


Design for Summation Problem (6/7)

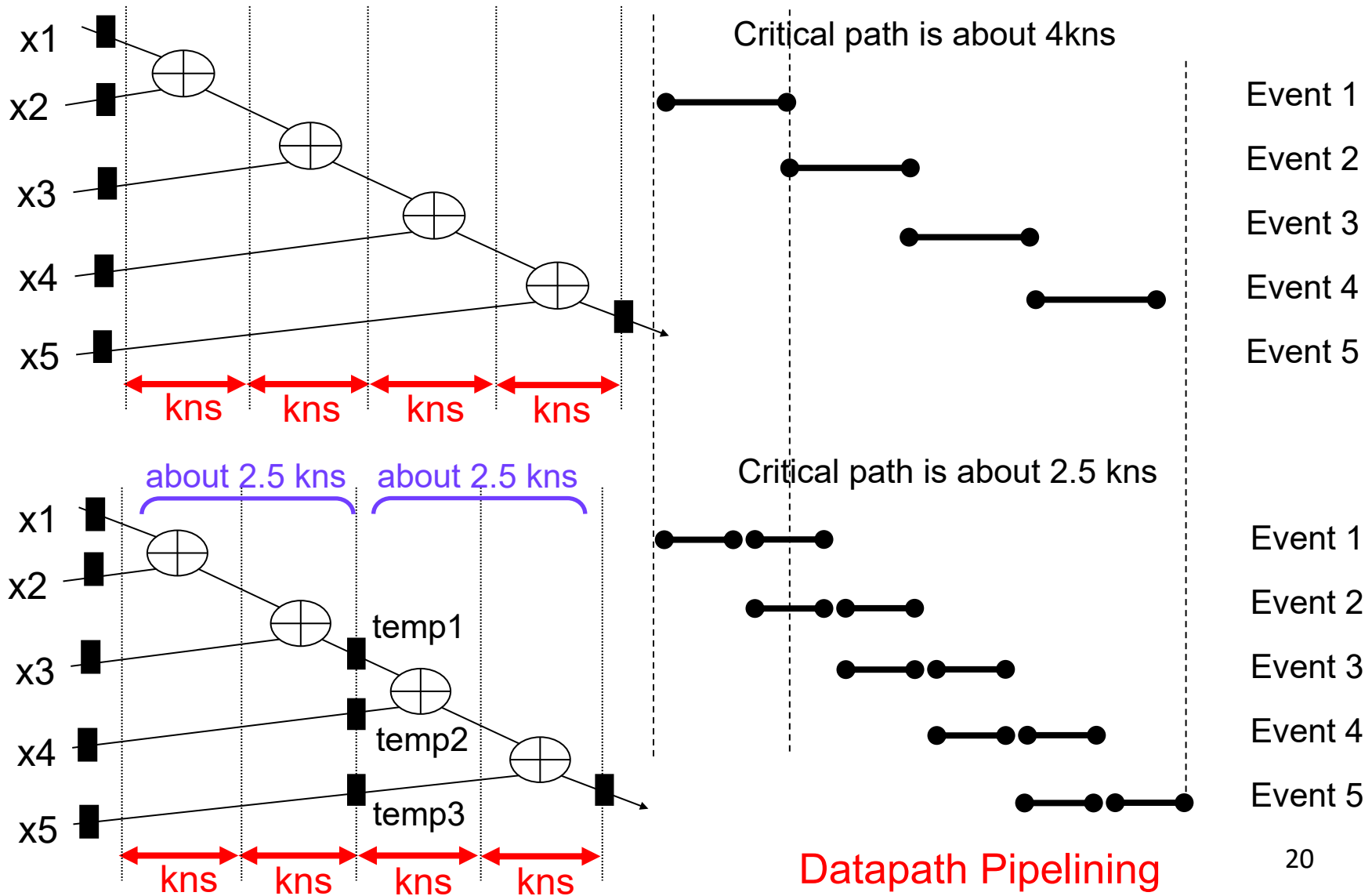

Design for Summation Problem (7/7)

 


Critical path is about 2.5 kns

 

Critical path is about 3.5 kns

Which one is better ? Balance is important

Optimization for RTL Design

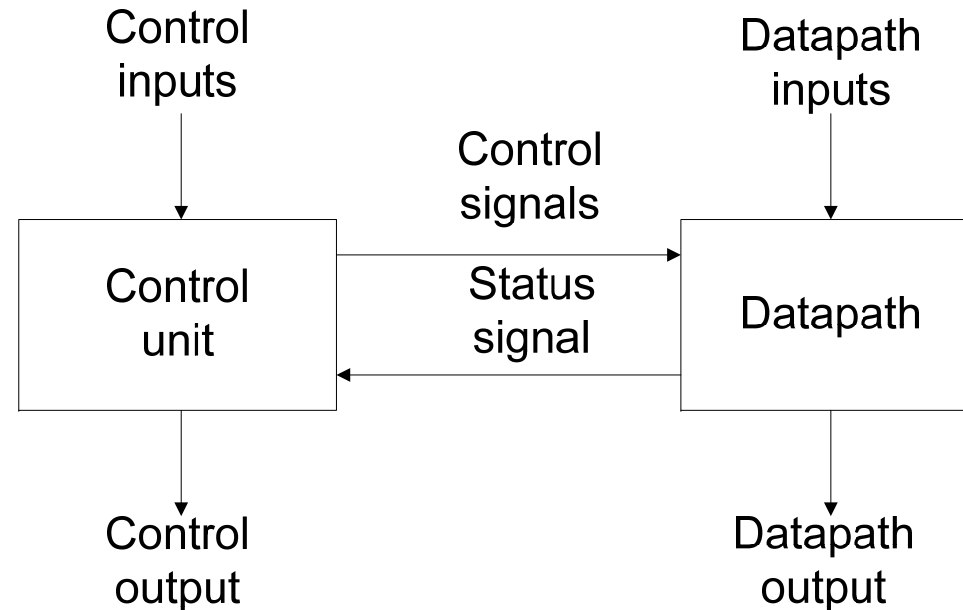

Optimization for control unit:

1. As suggestion by most textbooks of “Logic System Design”
2. Write HDL descriptions with good styles, and then optimized by EDA tools


Optimization for datapath:

1. Resource optimization
2. Time optimization

Optimization for Control Unit

Traditional Optimization Flow for Control Unit

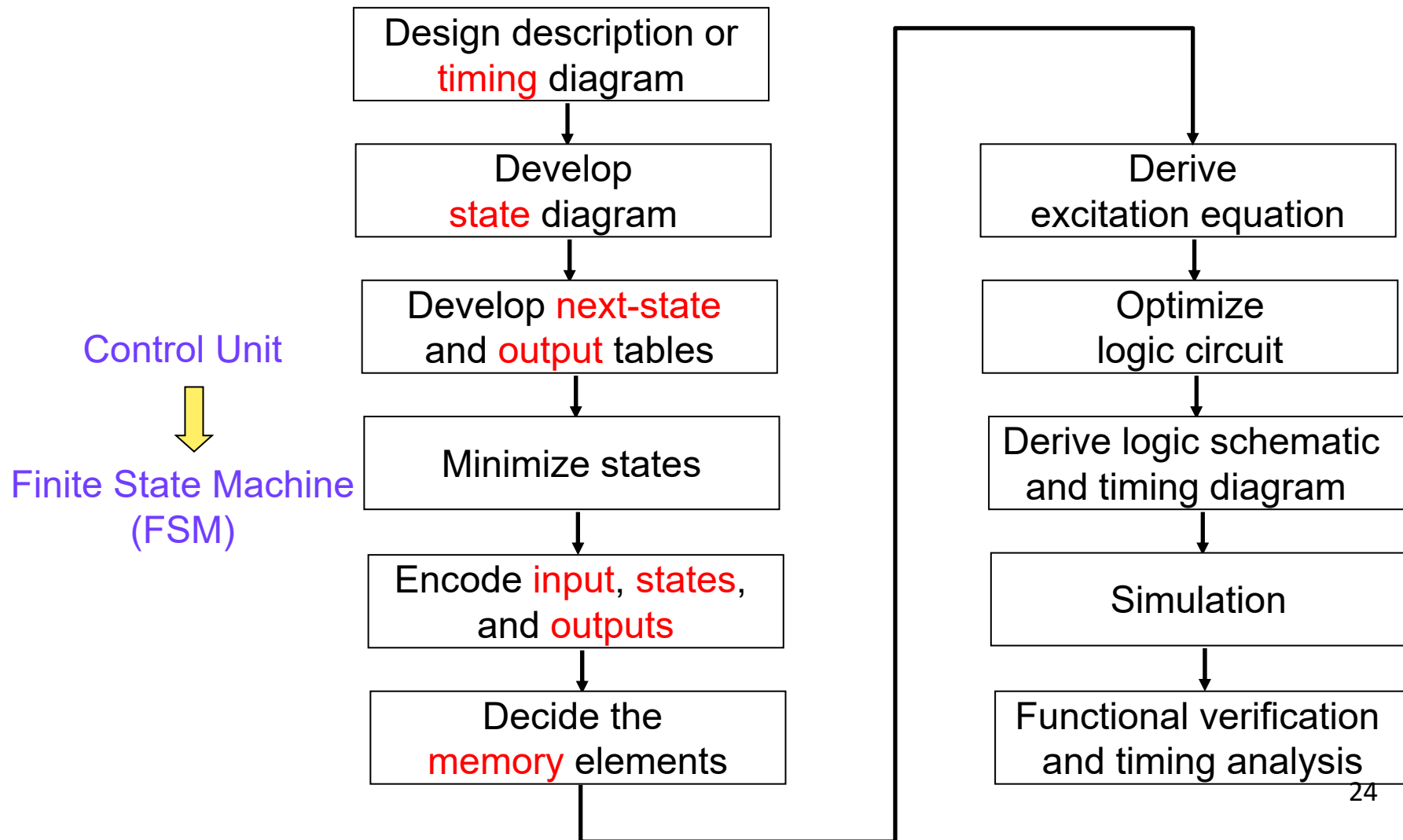=> Use Finite State Machine to design Control unit




Finite State Machine (1/4)

Moore machine: $S \rightarrow O$ (output is dependent only on current state)

Mealy machine: $S \times I \rightarrow O$ (output is dependent on input and state)

State diagram for a **Mealy** machine

Four states: S_0, S_1, S_2, S_3

 


Next-state and output tables (I=input)

Present State	Next State		Output	
	I=0	I=1	I=0	I=1
S_0	S_0	S_1	0	1
S_1	S_1	S_2	1	0
S_2	S_2	S_0	0	1
S_3	S_3	S_1	0	1


Finite State Machine (2/4)

$$S \rightarrow O$$

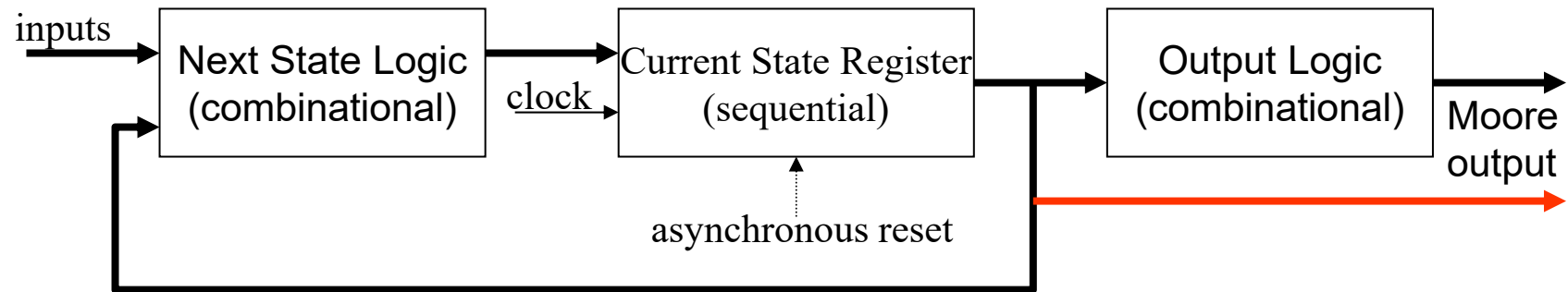

Moore Machine (state-based machine)


$$S \times I \rightarrow O$$

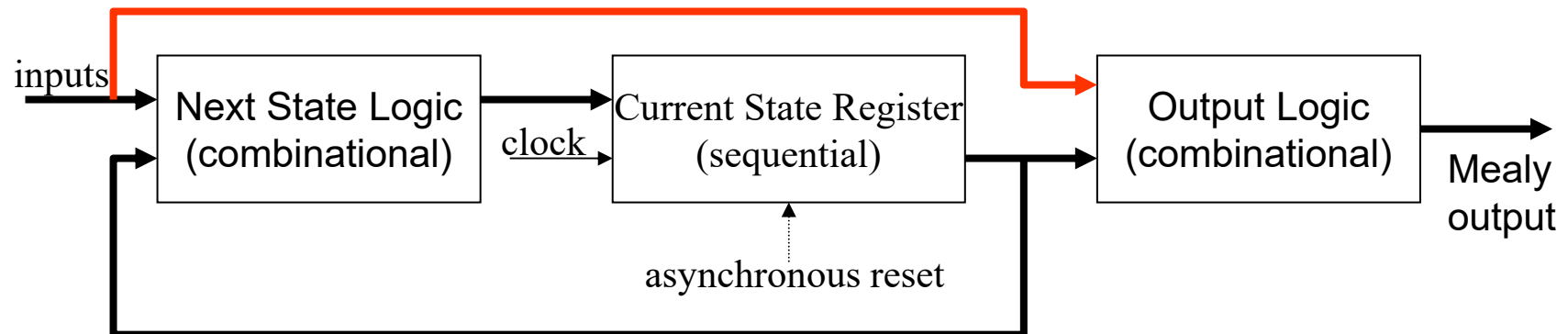

Mealy Machine (input-based machine)

Finite State Machine (3/4)

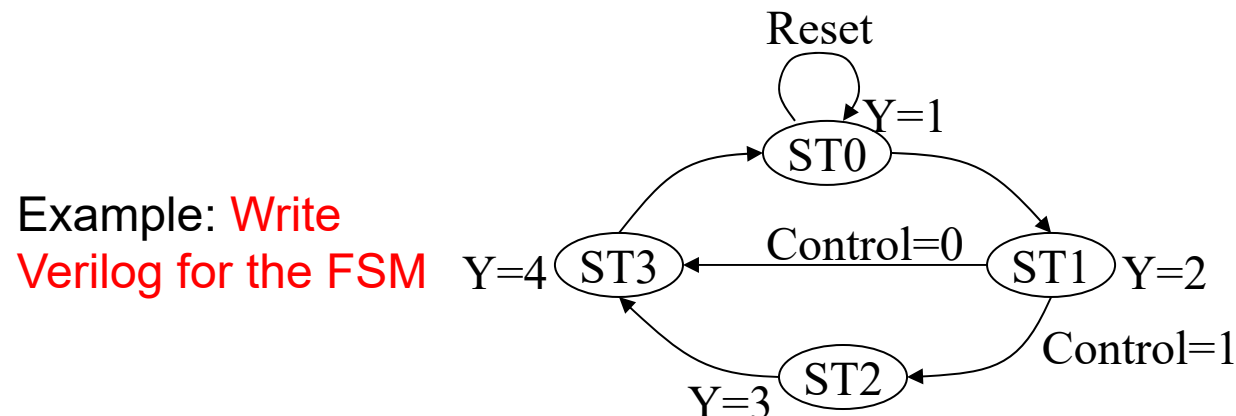- For best legibility, describe FSM using two or three *always@* statements
 - (1) *current* state or state register (sequential circuit)
 - (2) *next* state logic (combinational circuit)
 - (3) *output* logic (combinational circuit)
- Two combinational logic can be merged
- Use *parameter* to describe the state name



Review: State Encoding

- Common FSM encoding options:
 - One-hot code
 - Binary code
 - Gray code
 - Random code

State	Binary	Gray	One hot
<i>A</i>	00	00	1000
<i>B</i>	01	01	0100
<i>C</i>	10	11	0010
<i>D</i>	11	10	0001

Finite State Machine (4/4)

```
module FSM(Clock, Reset, Control, Y)
input Clock, Reset, Control;
output [2:0] Y;
```

```
reg [1:0] CurrentState, Nextstate;
reg [2:0] Y;
```

```
parameter [1:0] ST0 = 2'b00,
                ST1 = 2'b01,
                ST2 = 2'b10,
                ST3 = 2'b11;
```

State name
(parameter)

```
always @(posedge Clock or posedge Reset)
if (Reset)
```

```
    CurrentState <= ST0;
```

```
else
```

```
    CurrentState <= NextState;
```

State
register
(Seq.C.)

Next state
logic
(Comb.C.)

```
always @(Control or Currentstate)
begin
```

```
    NextState = ST0;
```

```
    case (CurrentState)
```

```
        ST0: NextState = ST1;
```

```
        ST1: if (Control)
```

```
            NextState = ST2;
```

```
        else
```

```
            NextState = ST3;
```

```
        ST2: NextState = ST3;
```

```
        ST3: NextState = ST0;
```

```
    endcase end
```

```
always @(CurrentState)
```

```
begin
```

```
    case(CurrentState)
```

```
        ST0: Y = 1; ST1: Y = 2;
```

```
        ST2: Y = 3; ST3: Y = 4;
```

```
    endcase
```

```
end endmodule
```


Output
logic
(Comb.C.)

Moore Machine (1/8)


$S \rightarrow O$ S :state O :output

Next-state and output tables (I =input)

Present State	Next State		Output	
	$I=0$	$I=1$	$I=0$ or 1	
S_0	S_0	S_2	0	
S_1	S_0	S_2	1	
S_2	S_2	S_3	1	
S_3	S_3	S_1	0	

 

Optimization flow


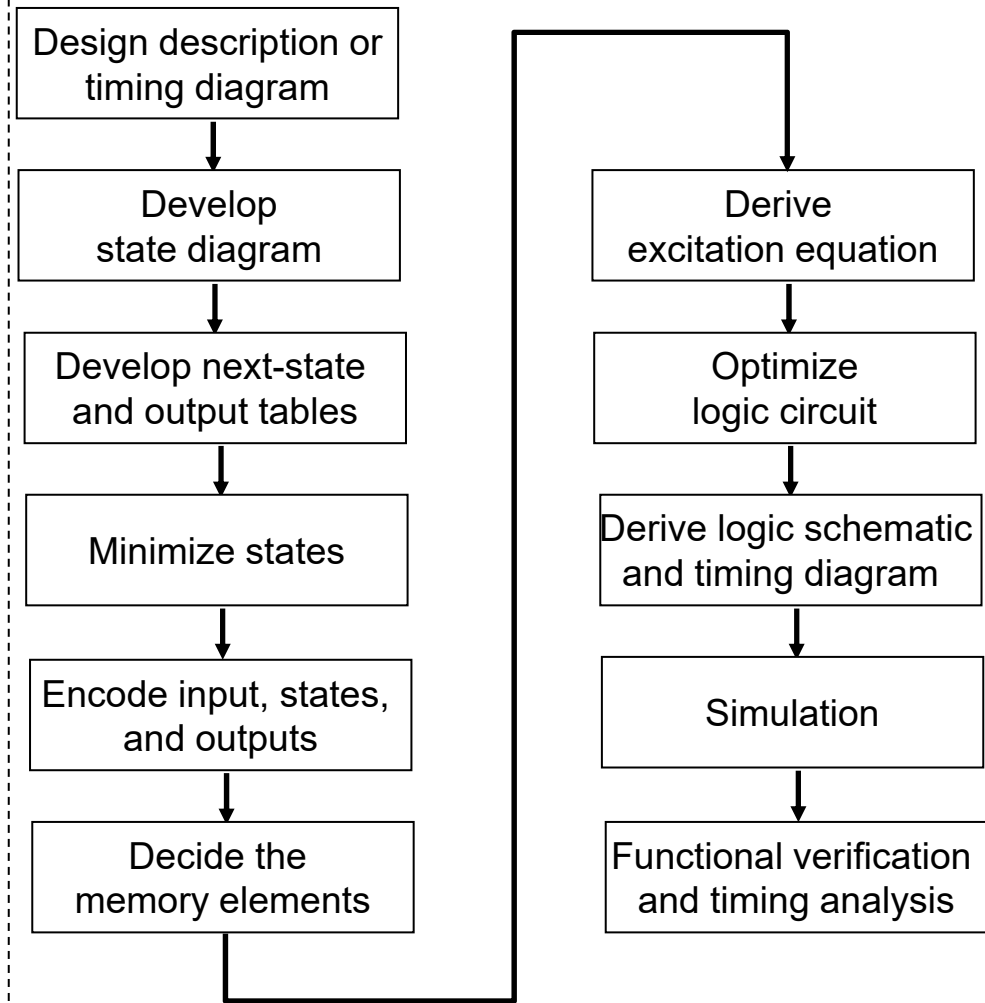


Moore Machine (2/8)

original state table

Present State	Next State		Output	
	I=0	I=1	I=0	I=1
S ₀	S ₀	S ₂	0	0
S ₁	S ₀	S ₂	1	1
S ₂	S ₂	S ₃	1	1
S ₃	S ₃	S ₁	0	0

  Assume that we use JK flip-flops for storage
4 states \Rightarrow need 2 flip-flops (named M and N)



characteristic table

J	K	Q(t+1)
0	0	Q(t)
0	1	0
1	0	1
1	1	Q'(t)

excitation table

Q(t)	Q(t+1)	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

I	Present State		Next State		M(JK)		N(JK)		Output
	M(t)	N(t)	M(t+1)	N(t+1)	MJ	MK	NJ	NK	
0	0	0	0	0	0	X	0	X	0
1	0	0	1	0	1	X	0	X	0
0	0	1	0	0	0	X	X	1	1
1	0	1	1	0	1	X	X	1	1
0	1	0	1	0	X	0	0	X	1
1	1	0	1	1	X	0	1	X	1
0	1	1	1	1	X	0	X	0	0
1	1	1	0	1	X	1	X	0	0

Moore Machine (3/8)

MN					
I \		00	01	11	10
0		0	0	X	X
1		1	1	X	X

$MJ=I$

MN					
I \		00	01	11	10
0		X	X	0	0
1		X	X	1	0

$MK=NI$

MN					
I \		00	01	11	10
0		0	1	0	1
1		0	1	0	1


$\text{Output}=M'N+MN'$

MN					
I \		00	01	11	10
0		0	X	X	0
1		0	X	X	1

$NJ=MI$



MN					
I \		00	01	11	10
0		X	1	0	X
1		X	1	0	X

$NK=M'$

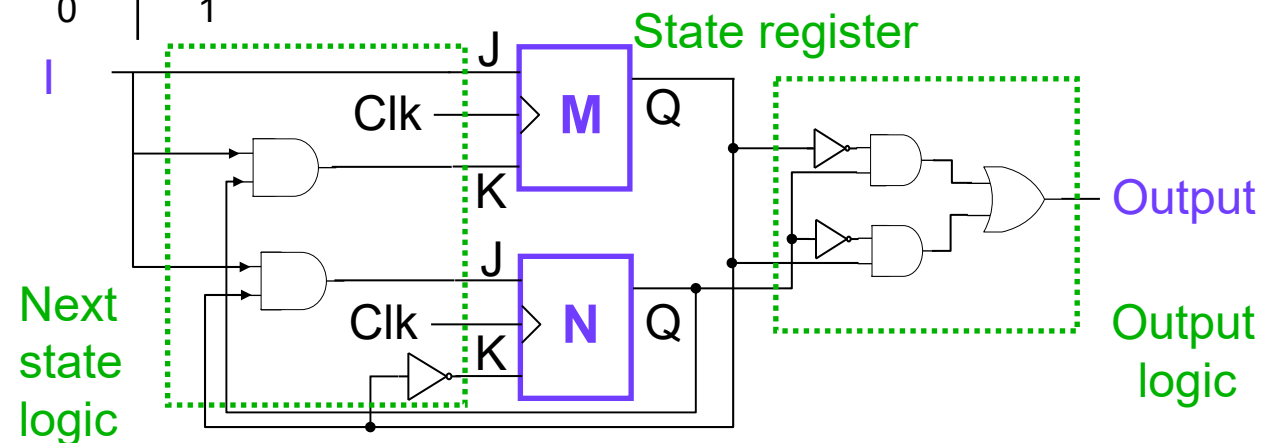


Moore Machine (4/8)

Synthesis Result

 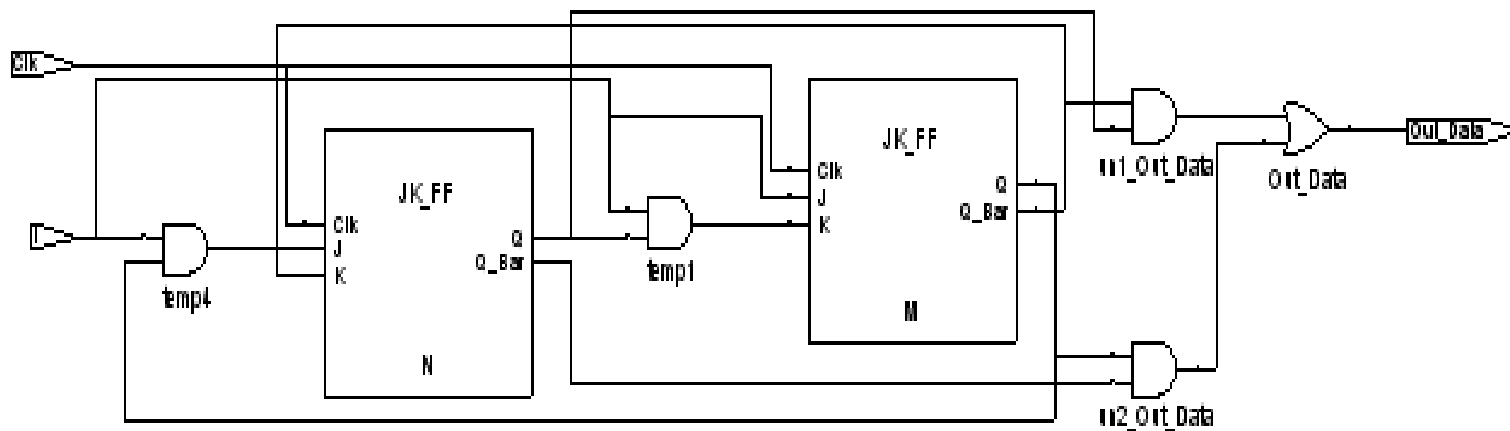

Implement the circuit with structural HDL, See circuit in the previous slide

Moore Machine (5/8)

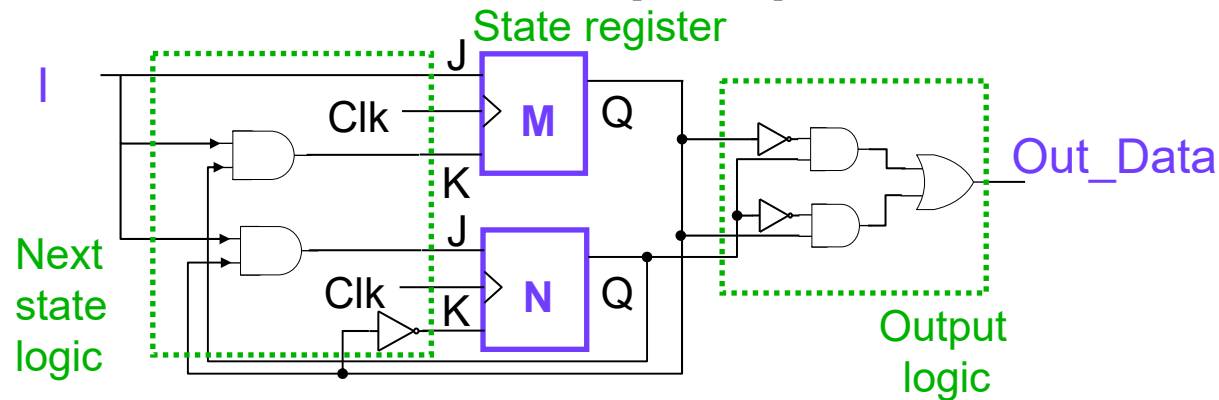

```

module moore_JK(Clk, I, Out_Data);
input  Clk, I; output Out_Data;
wire  temp1, temp2, temp3, temp4, temp5, temp6;
assign temp1 = I & temp5;
assign temp4 = I & temp2;
assign Out_Data = (temp3 & temp5) | (temp2 &
temp6);
JK_FF M(Clk, I, temp1, temp2, temp3);
JK_FF N(Clk, temp4, temp3, temp5, temp6);
endmodule

```

```

module JK_FF(Clk, J,
K, Q, Q_Bar);
input  Clk, J, K;
output Q, Q_Bar;
reg    Q, Q_Bar;
always @(posedge Clk)
begin
    case({J,K})
        2'b00:
            Q=Q;
        2'b01:
            Q=0;
        2'b10:
            Q=1;
        2'b11:
            Q=~Q;
    endcase
end
endmodule

```

The better way is to write behavioral HDL directly and let the EDA tool do the whole optimization job (including Karnaugh Map and logic minimization)

Moore Machine-Bad Example (6/8)

Both State and Out_Data are implemented with flip-flops

```
module moore_bad(Clk,
Reset, In_Data, Out_Data);
input  Clk, Reset, In_Data;
output [1:0] Out_Data;
reg    [1:0] Out_Data;
reg    [1:0] State;
parameter S0=2'b00,
S1=2'b01, S2=2'b11,
S3=2'b10;
always @(posedge Clk)
begin
    if(Reset)
        State=S0;
    else begin
        case(State)
```

```
        S0: begin
                Out_Data = 0;
                if(In_Data == 1)
                    State = S2;
                else
                    State = S0;
            end
        S1: begin
                Out_Data = 1;
                if(In_Data == 1)
                    State = S2;
                else
                    State = S0;
            end
        end
```

```
        S2: begin
                Out_Data = 1;
                if(In_Data == 1)
                    State = S3;
                else
                    State = S2;
            end
        S3: begin
                Out_Data = 0;
                if(In_Data == 1)
                    State = S1;
                else
                    State = S3;
            end
        endcase
    end
end
endmodule
```

Note: This is a bad-style HDL

Moore Machine-Good Example (7/8)

```
module moore_good(Clk,  
    Reset, In_Data, Out_Data);  
  
input Clk, Reset, In_Data;  
output [1:0] Out_Data;  
reg [1:0] Out_Data;  
reg [1:0] State, NextState;  
parameter S0=2'b00, S1=2'b01,  
    S2=2'b10, S3=2'b11;
```

```
always @(posedge Clk or  
    posedge Reset)  
begin  
    if(Reset)  
        State <= S0;  
    else  
        State <= NextState;  
end  
State register (flip-flops)
```



```
always @(In_Data or State)  
begin  
    case(State)  
        S0: begin  
            if(In_Data == 1)  
                NextState = S2;  
            else  
                NextState = S0;  
            end  
        S1: begin  
            if(In_Data == 1)  
                NextState = S2;  
            else  
                NextState = S0;  
            end  
        S2: begin  
            if(In_Data == 1)  
                NextState = S3;  
            else  
                NextState = S2;  
            end  
    endcase  
end
```

```
S3: begin  
    if(In_Data == 1)  
        NextState = S1;  
    else  
        NextState = S3;  
    end  
endcase  
end  
Next state logic
```

```
always @(State)  
begin  
    case(State)  
        S0: Out_Data = 0;  
        S1: Out_Data = 1;  
        S2: Out_Data = 1;  
        S3: Out_Data = 0;  
    endcase  
end  
endmodule  
Output logic
```

Note: This is a good-style HDL (only “State” is implemented with flip-flops)

Moore Machine-Good Example (8/8)

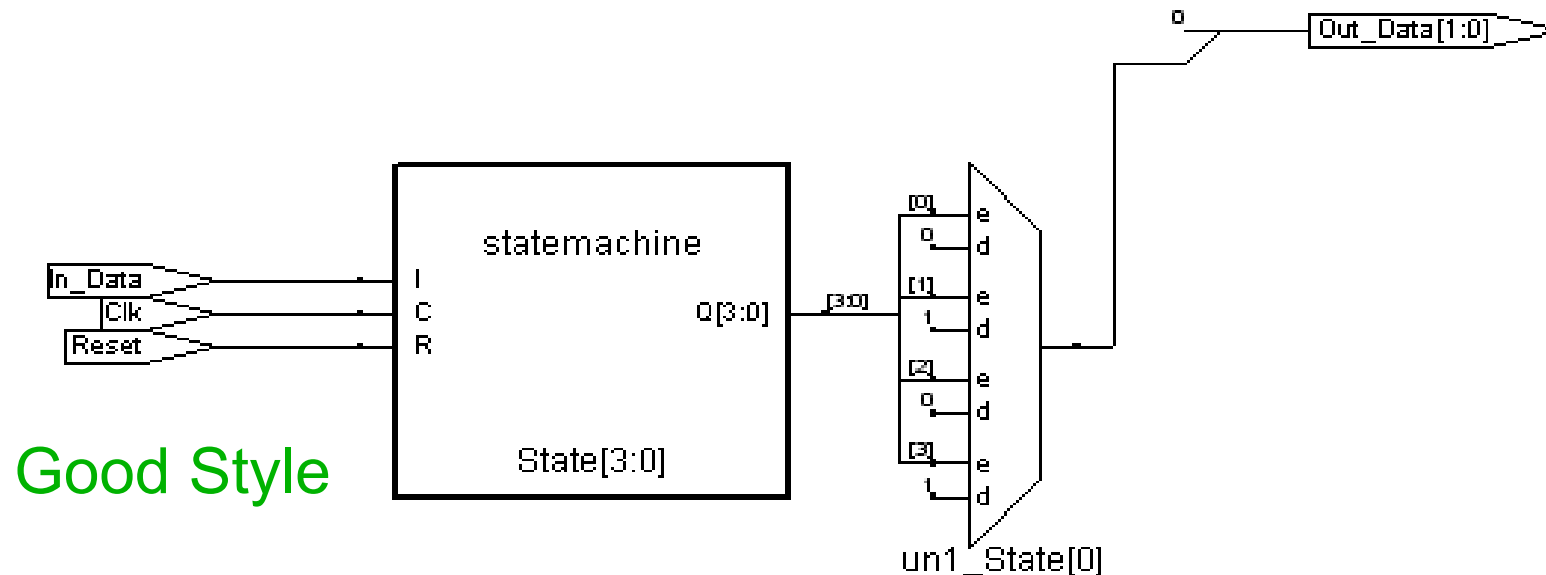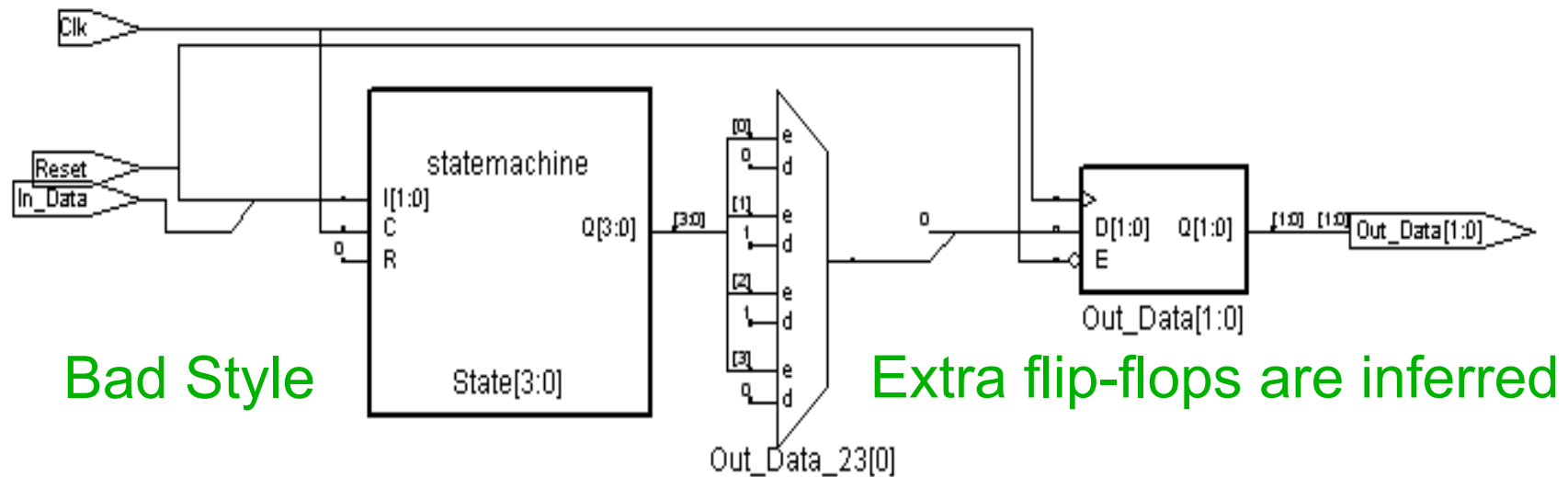


Mealy Machine (1/2)

State diagram

Four states: S_0 , S_1 , S_2 , S_3

Input/Output

 


Next-state and output tables (I =input)

Present State	Next State		Output	
	$I=0$	$I=1$	$I=0$	$I=1$
S_0	S_0	S_1	0	1
S_1	S_1	S_2	1	0
S_2	S_2	S_0	0	1
S_3	S_3	S_1	0	1

Mealy Machine (2/2)

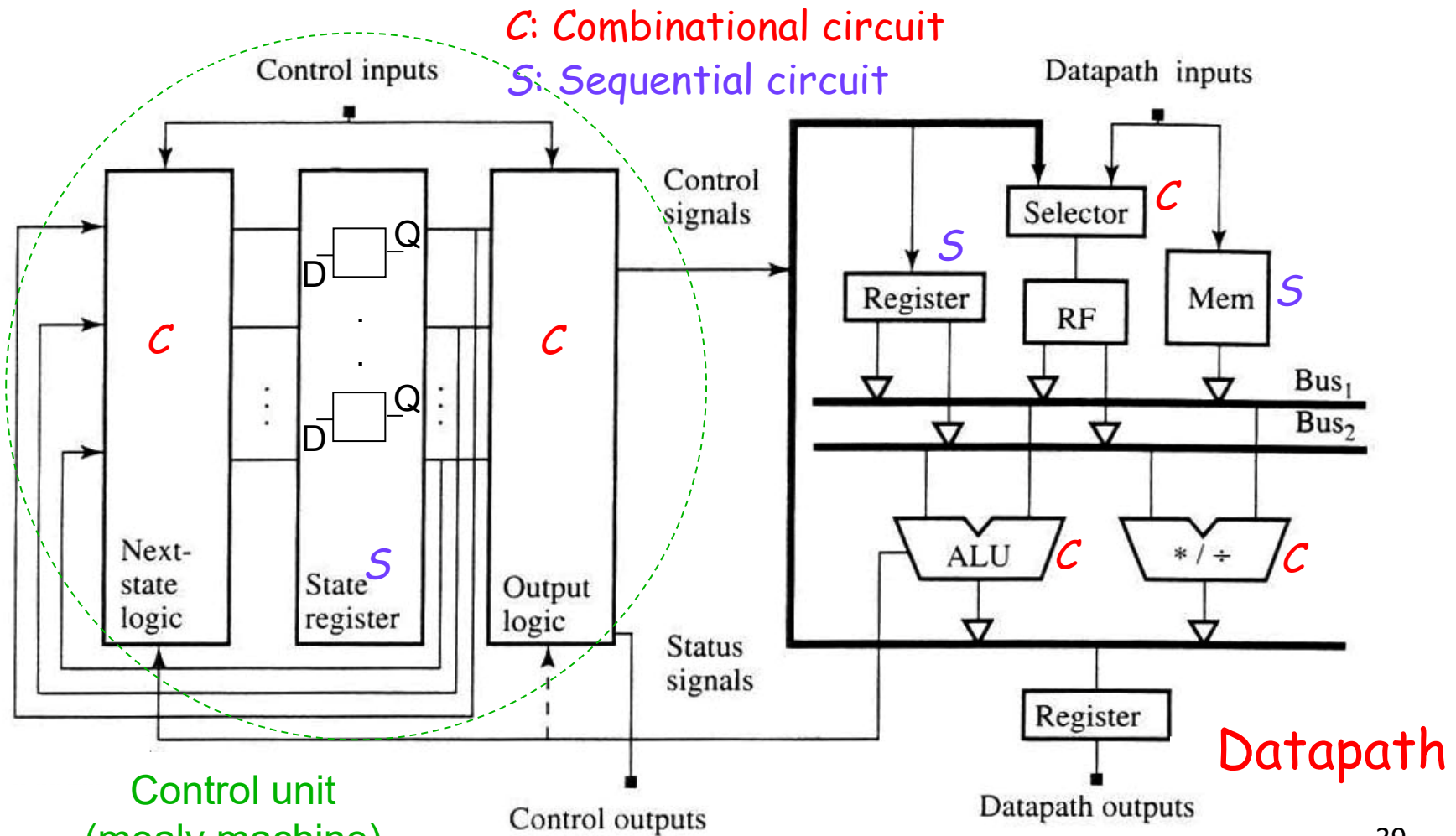
Remember to write your mealy machine by using the **good-style** HDL



Using **three always** statements

Control-Unit Implementation Styles (1/3)


Hardwired Control

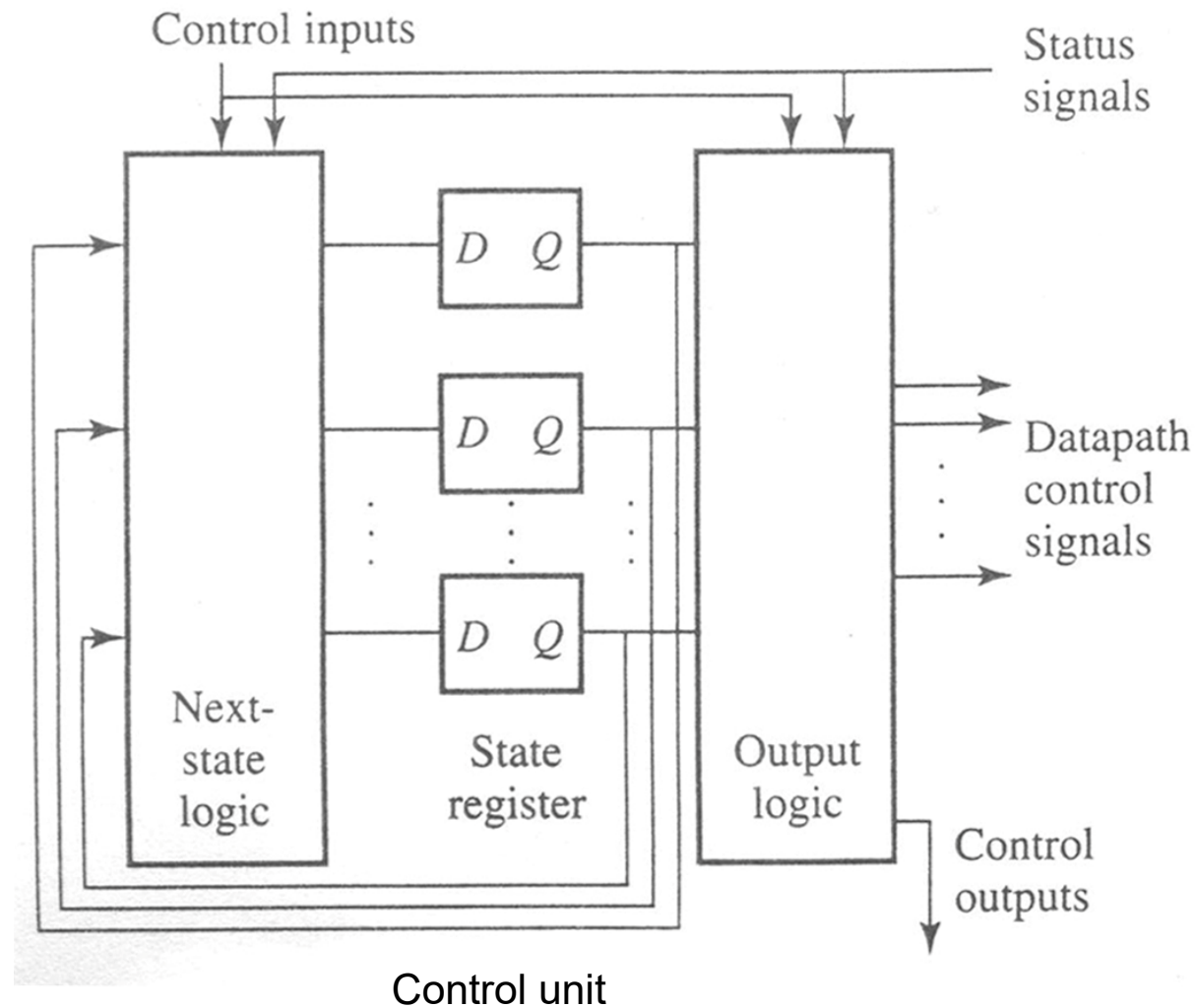

Control-Unit Implementation Styles (2/3)

Hardwired Control

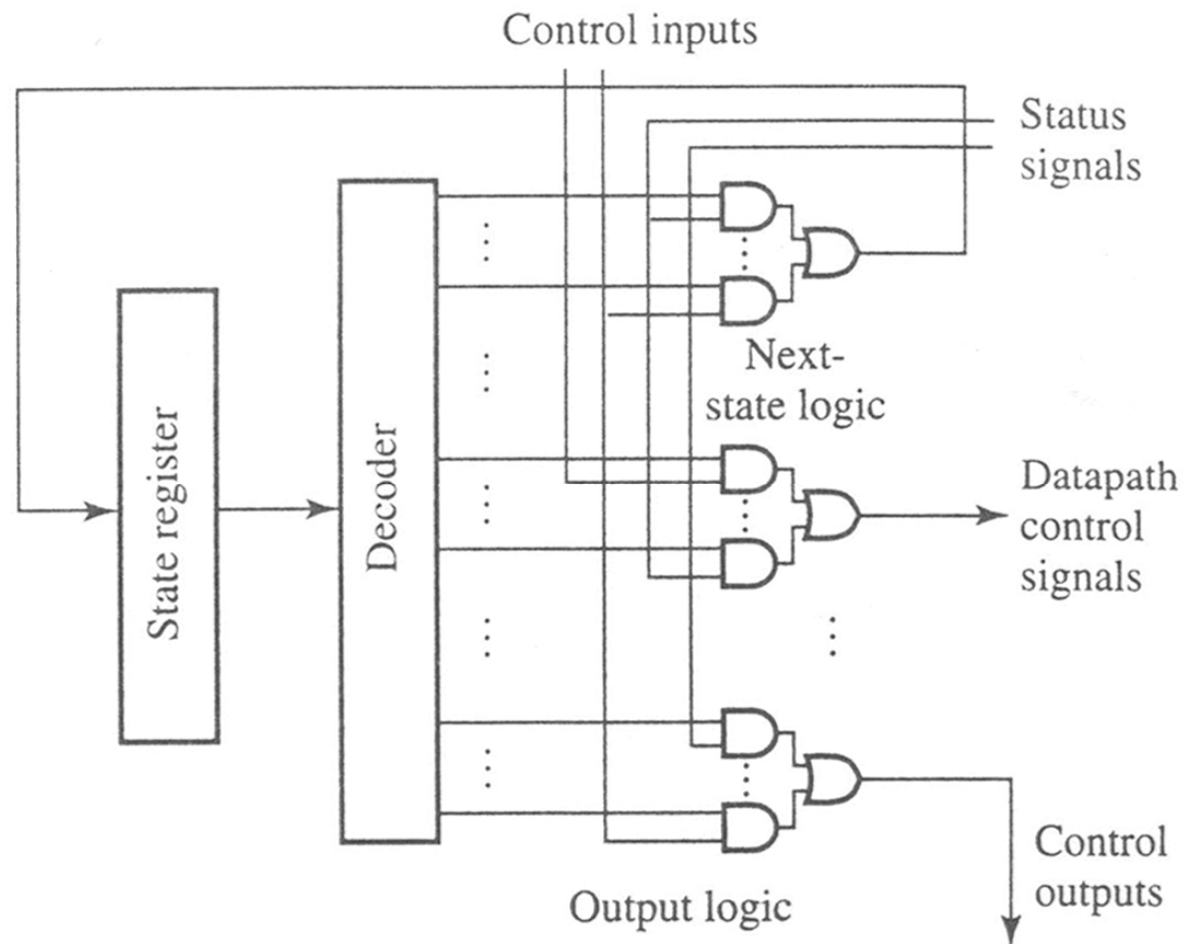
Control unit with state-register and decoder



Control unit with state-register and decoder

Control-Unit Implementation Styles (3/3)

Microprogramming
Control

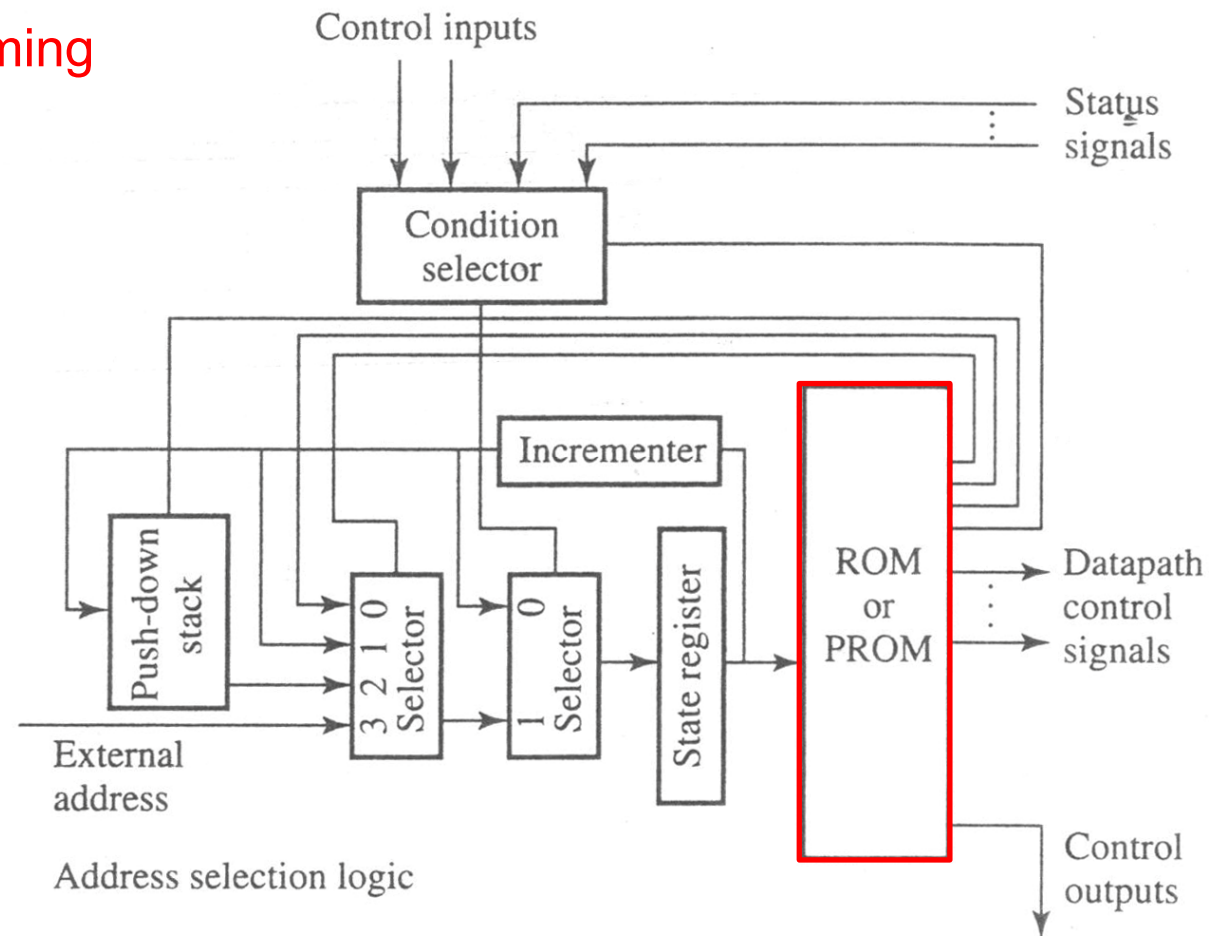


Control unit with state-register and ROM

Example


- Design a traffic light controller which has the following behavior
 - Two input signals (**Clock**, **Reset**) are for clock in and reset signal.
 - Three output signals (**Red**, **Yellow**, **Green**) enable each of red light, yellow light and green light.
 - The time with each traffic light is **5** seconds for red light, **3** seconds for green light and **1** second for yellow light.
 - The sequence of traffic light is in specific order (red, yellow, green and repeat).

Traffic Light Controller (1/7)

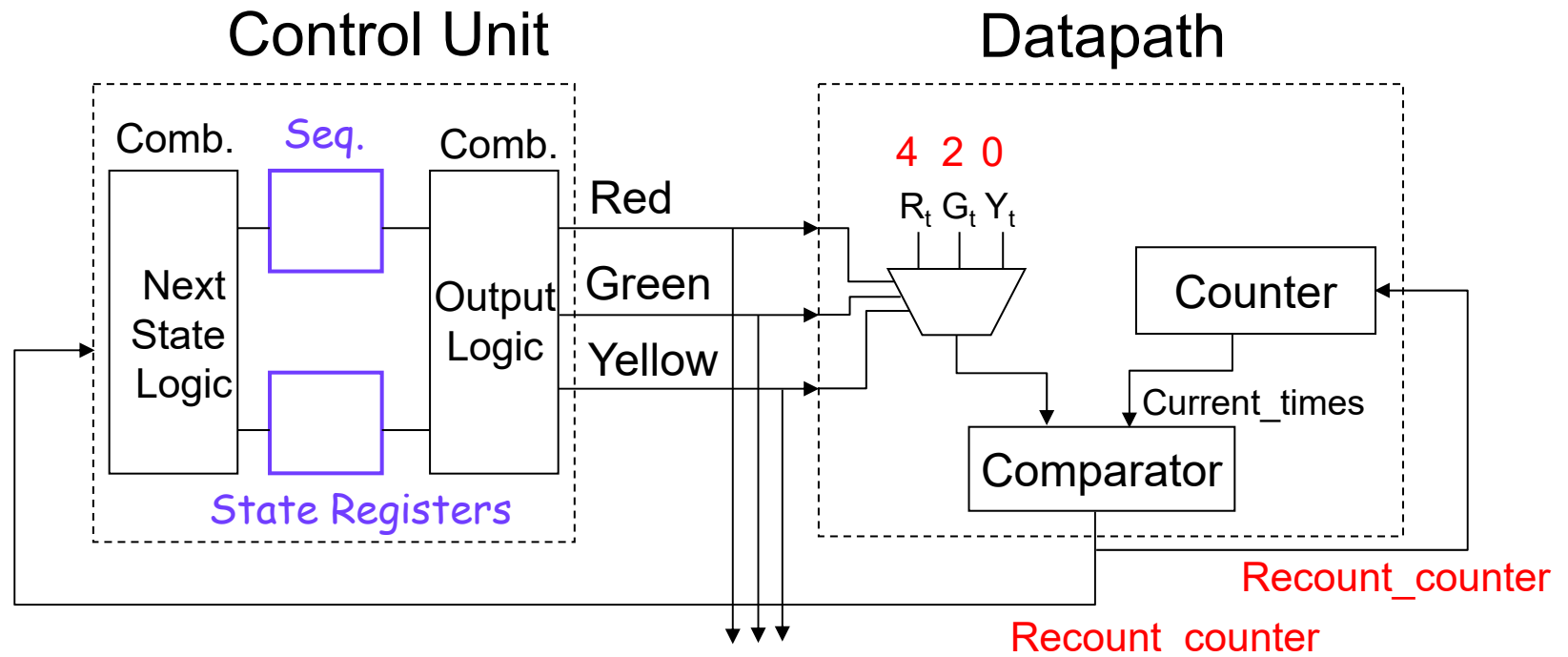

Input/Output

Recount_Counter16/Red Green Yellow

 

R_time: 4+1=5 cycles
 G_time: 2+1=3 cycles
 Y_time: 0+1=1 cycles

Traffic Light Controller (2/7)

```
module traffic(Clock,Reset,Red,Green,Yellow);  
input Clock,Reset; output Red,Green,Yellow;  
wire Recount_conter; wire [3:0]  
Counter_Number;
```

```
Traffic_Control (.Clock(Clock),.Reset(Reset),  
.Recount_Counter16(Recount_conter),.Red(Red),  
.Green(Green),.Yellow(Yellow));
```

```
Datapath  
(.Clock(Clock), .Reset(Reset), .RGY({Red,Green,  
n,Yellow}), .Recount(Recount_conter));  
endmodule
```

```
module Datapath(Clock, Reset, RGY,  
Recount);  
input Clock, Reset; input [2:0] RGY;  
output Recount; wire [3:0] Counter_Number;
```

```
Compare A1  
(.current_times(Counter_Number),  
.RGY(RGY), .Recount_conter16(Recount)  
);  
Counter16 A2 (.Clock(Clock),.Reset(Reset),  
.Recount_Counter16(Recount), .Count_Out(Counter_Number));  
  
endmodule
```

Traffic Light Controller (3/7)

```
module Counter16(Clock,Reset,Recount_Counter16,  
                 Count_Out);  
input Clock,Reset,Recount_Counter16;  
output [3:0] Count_Out;  
reg [3:0] Count_Out;  
  
always@(posedge Clock)  
begin  
    if(Reset)  
        Count_Out=0;  
    else  
        begin  
            if(Recount_Counter16)  
                Count_Out=0;  
            else  
                Count_Out=Count_Out+1;  
        end  
    end  
end  
endmodule
```

Traffic Light Controller (4/7)

```
module compare(current_times,  
RGY, Recount_conter16);  
input [2:0] RGY;  
input [3:0] current_times;  
output Recount_conter16;  
reg Recount_conter16;  
parameter R_times=4, G_times=2,  
Y_times=0;  
  
always @(RGY)  
begin  
    case(RGY)  
        3'b100:begin  
            if(current_times == R_times)  
                Recount_conter16=1;  
            else  
                Recount_conter16=0;  
            end  
    end
```

```
        3'b001:begin  
            if(current_times == Y_times)  
                Recount_conter16=1;  
            else  
                Recount_conter16=0;  
            end  
        3'b010:begin  
            if(current_times == G_times)  
                Recount_conter16=1;  
            else  
                Recount_conter16=0;  
            end  
        default: Recount_conter16=1;  
    endcase  
end  
endmodule
```


Traffic Light Controller (5/7)

```
module Traffic_Control(Clock,Reset,
    Recount_Counter16,Red,Green,Yellow);
input Clock, Reset,Recount_Counter16;
output Red, Green, Yellow;
reg Red, Green, Yellow;
reg [1:0] currentstate,nextstate;

parameter [1:0] Red_Light=0, Green_Light=1,
    Yellow_Light=2;

always@(posedge Clock)
begin
    if(Reset)
        currentstate = Red_Light;
    else
        currentstate = nextstate;
end
```

State Register (Seq. C.)

```
always@(currentstate)
begin
    case(currentstate)
        Red_Light:begin
            if(Recount_Counter16)
                nextstate=Green_Light;
            else
                nextstate=Red_Light; end
        Green_Light:begin
            if(Recount_Counter16)
                nextstate=Yellow_Light;
            else
                nextstate=Green_Light; end
        Yellow_Light:begin
            if(Recount_Counter16)
                nextstate=Red_Light;
            else
                nextstate=Yellow_Light; end
        default: nextstate=Red_Light;
    endcase
end
```

Next State Logic (Comb. C.)⁶⁴


Traffic Light Controller (6/7)

```
always @(currentstate)
begin
  case(currentstate)
    Red_Light:begin
      Red=1'b1;
      Green=1'b0;
      Yellow=1'b0;
    end
    Green_Light:begin
      Red=1'b0;
      Green=1'b1;
      Yellow=1'b0;
    end
    Yellow_Light:begin
      Red=1'b0;
      Green=1'b0;
      Yellow=1'b1;
    end
  end
end

default:begin
  Red=1'b0;
  Green=1'b0;
  Yellow=1'b0;
end
endcase
end
endmodule
```

Output Logic (Comb. C.)

Y_time: $0+1=1$ cycles

 



Backup slides