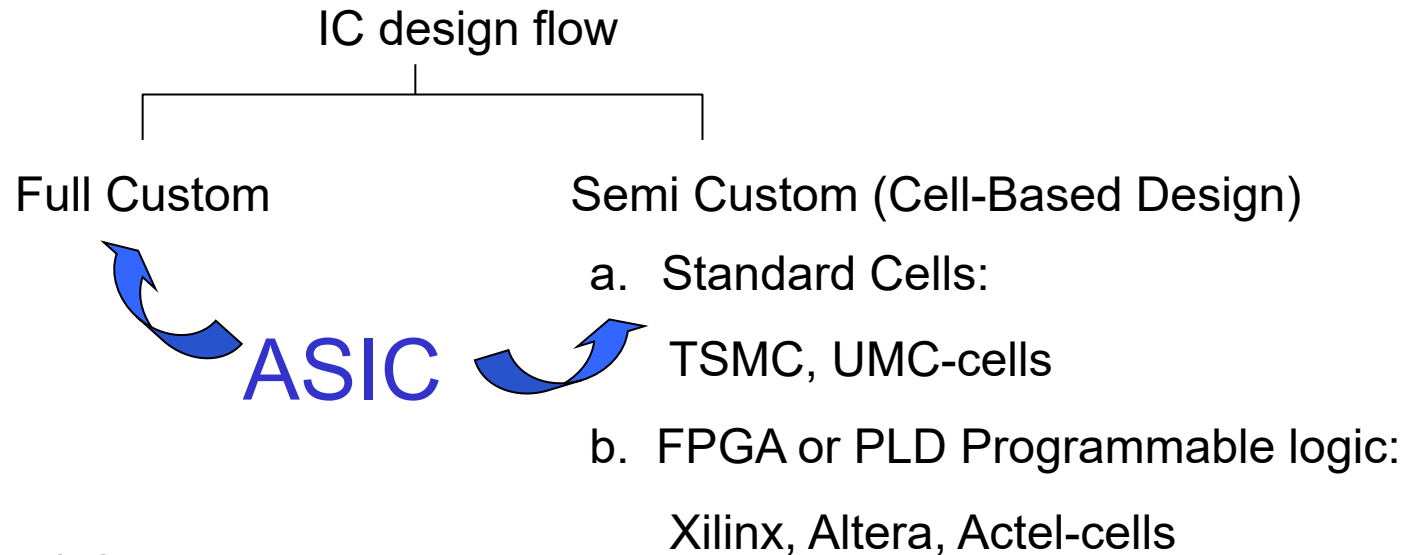


# IC Design Flow and RTL Coding

Slides modified from Prof. Pei-yin  
Chen's slides for Digital IC Design

# IC Design flow



Full (Fully) Custom Design:

- a. For analog circuits and digital circuits requiring custom optimization
- b. Gates, transistors and layout are designed and optimized by the engineer



Semi Custom Design:

- a. For larger digital circuits
- b. Real gates, transistors and layout are synthesized and optimized by related software tools
- c. Realization with hardware description language (HDL) such as VHDL and Verilog
  
# Full Custom Design

---

- Digital circuits requiring custom optimization (smaller system)
- Analog circuits
- When no CPLD or FPGA solutions available
- Cons: Long design cycle (transistors and wires)




# Semi Custom Design

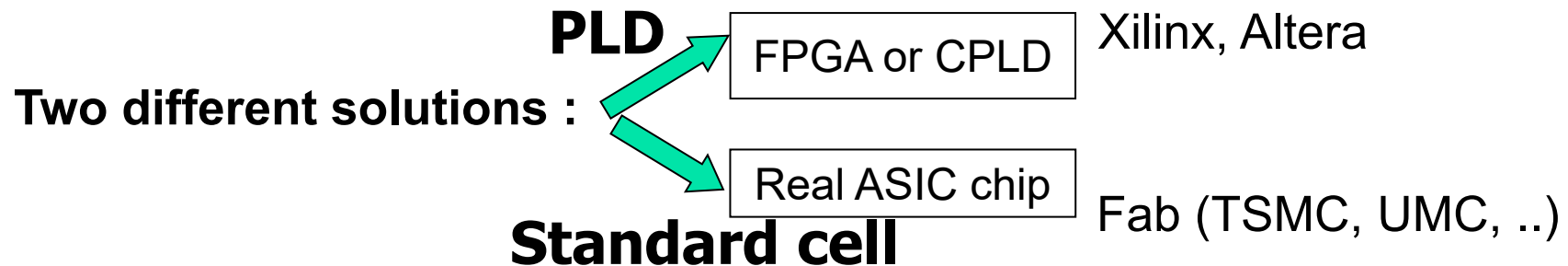- a. Product specification
- b. Modeling with HDL
- c. Synthesis (by using suitable standard cell)
- d. Simulation and verification
- e. Physical placement and layout
- f. Tape-out (real chip) -- implemented by suitable Fab companies
- g. Testing -- implemented by suitable tools and mechanisms

-- implemented with suitable tools

*more flexible, shorter design cycle, suitable for smaller production*



*less flexible, long design cycle, larger-scale production to reduce price*

# Standard Cells

---


## Standard Cell

- Cells are characterized and stored in **library**
- Need update when technology advance
- Need technology mapping before layout for each design

## Macro Cells


- Need parametrized capability in terms of speed and layout
- Examples : **FARADAY Memory Compiler**  
User Interface : memaker  
Single port RAM, Dual port RAM, ROM  
Data sheet, Verilog simulation module, netlist simulation timing
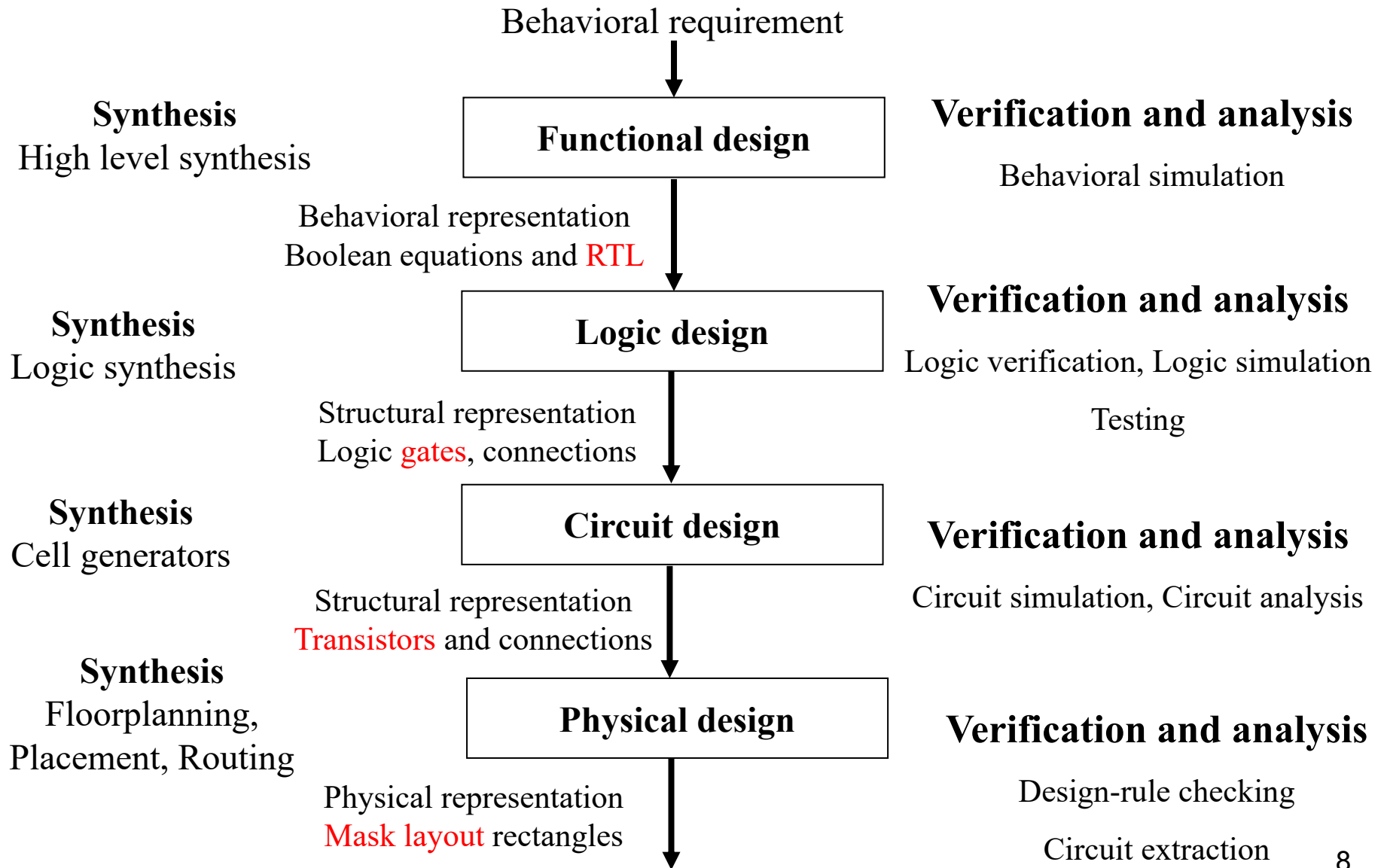
# Synthesis Flow of Semi Custom design (1/2)




# Synthesis Flow of Semi Custom design (2/2)


Functional design

 


Logic design

 

Circuit design

 

Physical design


 


# Logic Synthesis



- Synthesis = Translation + Optimization + Mapping

```
always @(...)  
  if (a==b)  
    if (c==1)  
      d=f;  
    else  
      d=1;  
  else  
    d=0;
```

**HDL Source**

  

  
**Translate into Boolean Representation**



 **Optimize + Map for target technology**

- Synthesis is **constraint-driven**

- You set the goals. Design Compiler optimizes design toward goals.





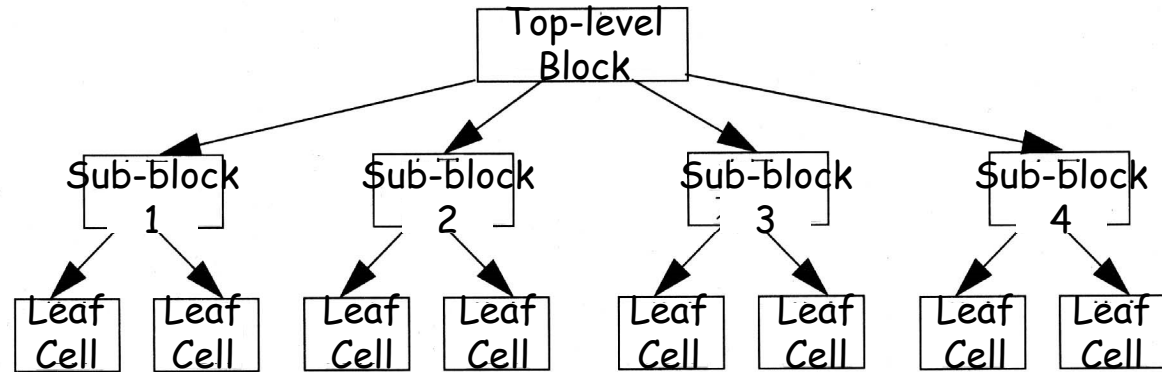
# Design Methodology

- Top-down

- Define the top-level block and identify the sub-blocks




Top-down design Methodology

- Bottom-up



- Identify the building blocks first and combine the blocks to bigger blocks

 - A combination of top-down and bottom-up flows is **typically** used.



Bottom-up design Methodology
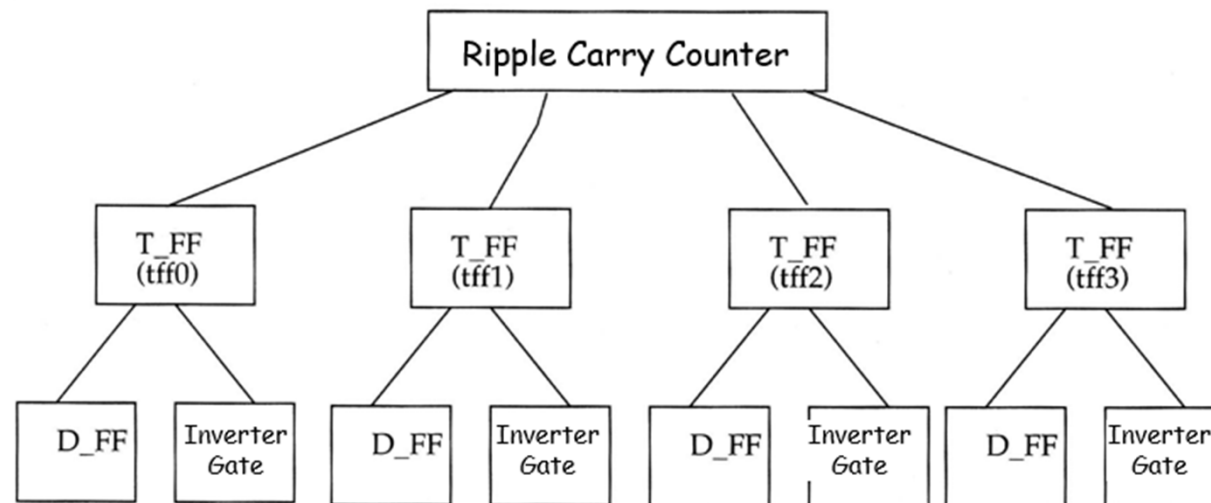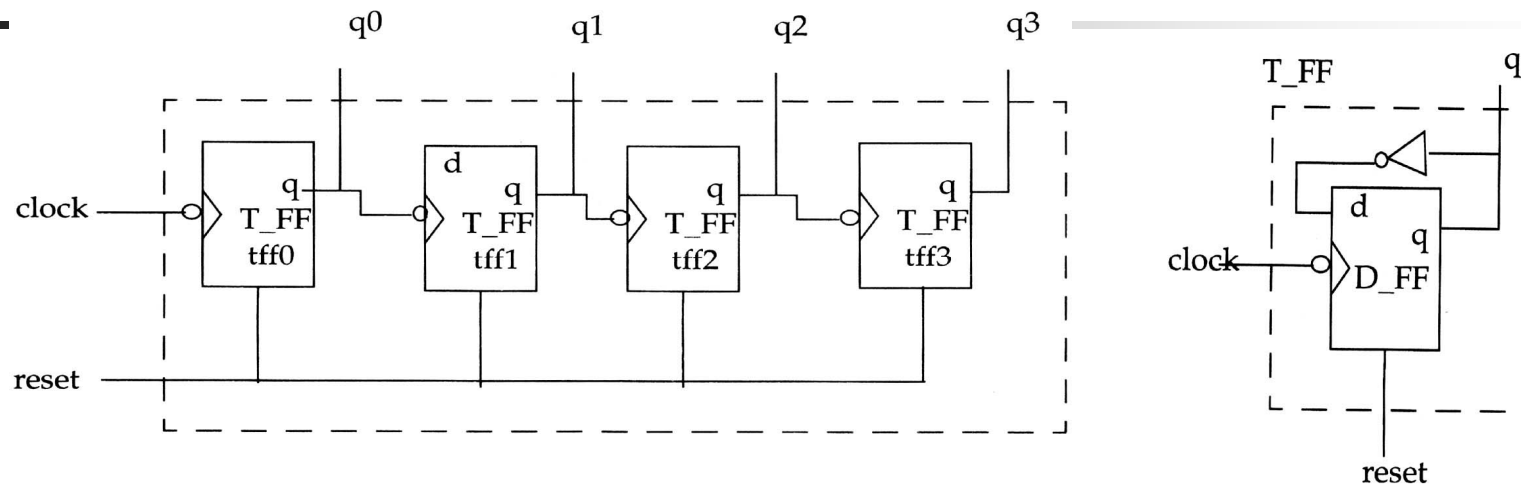
# Design Hierarchy of 4-bit Ripple Carry Counter



# Verilog Features

---

- Hardware description language allows you to describe circuit
- Procedural constructs for conditional, if-else, case and looping operations
- Arithmetic, logical, bit-wise, and reduction operations for expression
- Timing control

## Basics of Verilog Language:


- |                    |              |            |
|--------------------|--------------|------------|
| - Verilog Module   | - Identifier | - Keyword  |
| - Four Value Logic | - Data Types | - Numbers  |
| - Port Mapping     | - Operator   | - Comments |

# Verilog Module (1/2)

---

**Module** is the basic building block

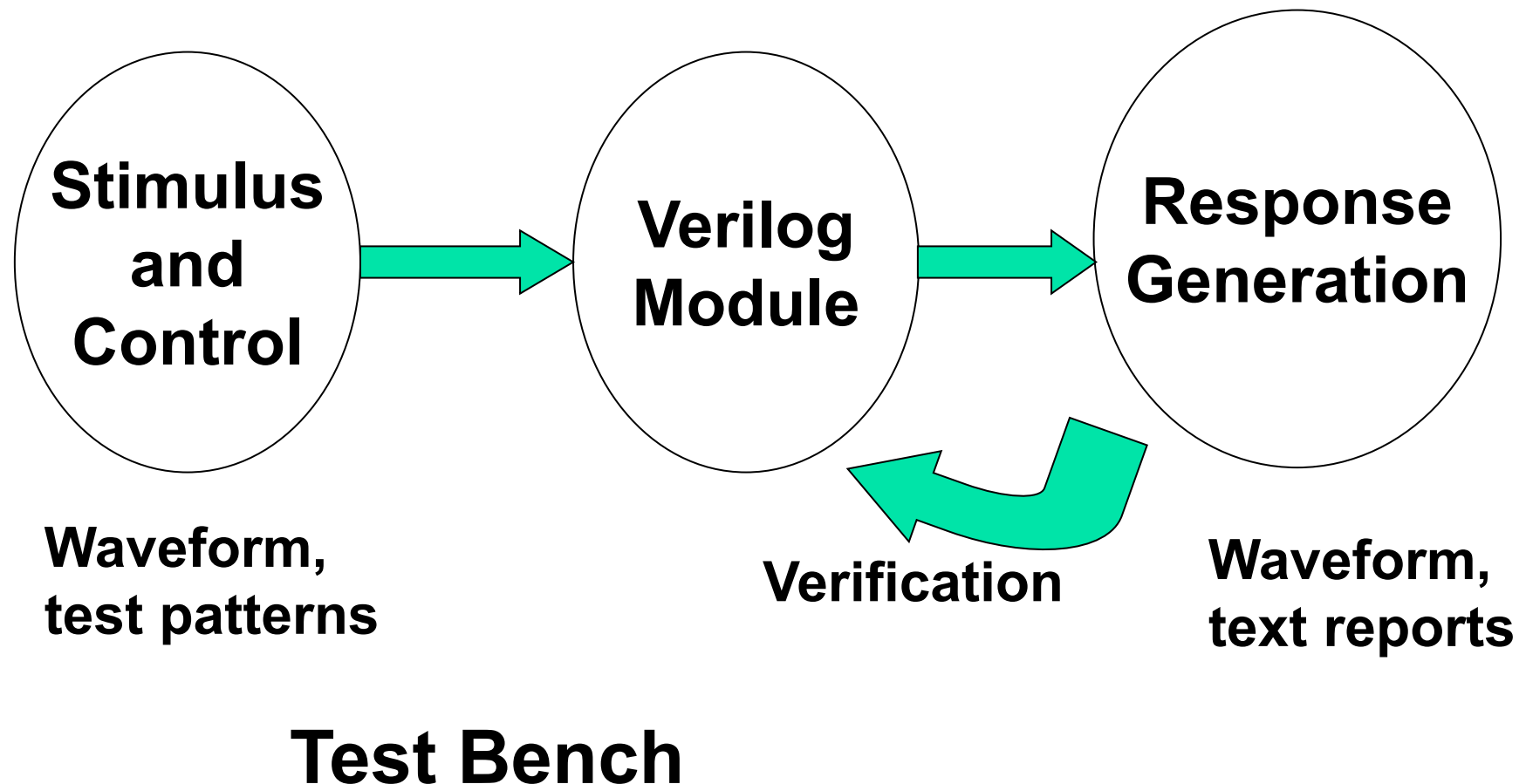An element, or a collection of lower-level blocks



# Verilog Module

**Module** is the basic building block

An element, or a collection of lower-level blocks


```
module module_name (port_name);
```

(1) port declaration

(2) data type declaration

(3) module functionality or structure

```
endmodule
```

 

```
module Add_half(sum, c_out, a, b);
```

(1) input a, b;  
output sum, c\_out;

(2) wire c\_out\_bar;

xor (sum, a, b);

(3) nand (c\_out\_bar, a, b);

not (c\_out, c\_out\_bar);

```
endmodule
```

# Three Different Circuit Descriptions

**Verilog allows three kinds of descriptions for circuits:**

- (1) **Structural** description
- (2) **Data flow** description
- (3) **Behavioral** description

**Structural description:**

1. module OR\_AND\_STRUCTURAL(IN,OUT);

2. input [3:0] IN;

3. output OUT;


4. wire [1:0] TEMP;

5. or u1(TEMP[0], IN[0], IN[1]);

6. or u2(TEMP[1], IN[2], IN[3]);

7. and (OUT, TEMP[0], TEMP[1]);

8. endmodule

 


 ***Synthesized (synthesis) + optimized by tools***

# Data Flow Description

## Data flow description

```
1. module OR_AND_DATA_FLOW(IN, OUT);  
2.   input      [3:0]      IN;  
3.   output                                OUT;  
4.   assign OUT = (IN[0] | IN[1]) & (IN[2] | IN[3]);  
endmodule
```

 ***Synthesized and  
optimized by tools***



***NOTE:***

What is the difference between C and Verilog?

C: only one iteration (once) is implemented for assignment


Verilog: hard-wired circuit for assignment

# Behavioral (RTL) Description (1/2)

---

## Behavioral description #1


```
1. module OR_AND_BEHAVIORAL(IN, OUT);  
2.   input [3:0]  IN;  
3.   output      OUT;  
4.   reg         OUT;  
  
5.   always @(IN  
6.   begin  
7.     OUT = (IN[0] | IN[1]) & (IN[2] | IN[3]);  
8.   end  
9. endmodule
```

 

**Activate OUT while any voltage transition  
(0→1 or 1→0) happens at signal IN**



# Behavioral (RTL) Description (2/2)

 

Truth Table

IN[0]	IN[1]	IN[2]	IN[3]	OUT
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	0
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

## Behavioral description #2

```
module or_and(IN, OUT);
```

```
input [3:0] IN; output OUT; reg OUT; (Note)
```

```
always @(IN)
```

```
begin
```

```
case(IN)
```

```
4'b0000: OUT = 0; 4'b0001: OUT = 0;
```

```
4'b0010: OUT = 0; 4'b0011: OUT = 0;
```

```
4'b0100: OUT = 0; 4'b0101: OUT = 1;
```

```
4'b0110: OUT = 1; 4'b0111: OUT = 1;
```

```
4'b1000: OUT = 0; 4'b1001: OUT = 1;
```

```
4'b1010: OUT = 1; 4'b1011: OUT = 1;
```

```
4'b1100: OUT = 0; 4'b1101: OUT = 1;
```

```
4'b1110: OUT = 1; default: OUT = 1;
```

```
endcase
```

```
end
```

```
endmodule
```

***Synthesized and  
optimized by tools***

# Instantiation and Instances

- Instantiation: the process of creating objects from a module
  - The objects are call **instances**
- No nesting is allowed

```
module ripple_carry_counter(q, clk, reset);  
  
output [3:0] q;  
input clk, reset;  
  
//4 instances of the module TFF are created.  
T_FF tff0(q[0],clk, reset);  
T_FF tff1(q[1],q[0], reset);  
T_FF tff2(q[2],q[1], reset);  
T_FF tff3(q[3],q[2], reset);  
  
endmodule
```

Create four  
T\_FF  
instances

```
module TFF(q, clk, reset);  
output q;  
input clk, reset;  
wire d;  
D_FF dff0(q, d, clk, reset);  
not n1(d, q); //  
endmodule
```

Instance  
name

Create  
D\_FF  
instances

# Structural Description for Cell-Based Implementation

---

Structural description (cell-based):

```
module OR_AND_STRUCTURAL(IN,OUT);
```

```
input      [3:0]    IN;  
output                                OUT;  
wire       [1:0]    TEMP;
```

```
orf203    u1(TEMP[0], IN[0], IN[1]);  
orf203    u2(TEMP[1], IN[2], IN[3]);  
andf201   (OUT, TEMP[0], TEMP[1]);  
endmodule
```

**Cell library** from:  
IBM, TSMC, UMC,...

**This kind of design is not portable. Why ?**

**Bad design method !**

# Difference Between C and Verilog

C language:



```
k=a+b;  
d=k+e;
```

Only executed once

Verilog language:

```
k=a+b;  
d=k+e;
```

or

  

**Two adders**  
(higher cost, higher speed)

**One adder**  
(lower cost, lower speed)  
clock rate might be faster

In Verilog, the output is generated using hardware. As long as inputs change, the output changes

# Identifier vs. Keyword


---

- **Identifiers** are names given to Verilog objects
- **Names** of modules, ports and instances are all identifiers
- First character must use a **letter**, and other character can use letter, number or “\_”
- Upper case and lower case letters are different
- **Predefined identifiers** to define the language constructs
- All keywords are defined in lower case
- Cannot be used as identifiers


Example:  
m\_y\_identifier  
\_myidentifier\$

Examples:  
module, initial, assign,  
always,  
endmodule, ...


# Four Value Logic

 


0: logic 0 / false

 

X: unknown logic value

 

1: logic 1 / true

 

Z: high-impedance

Number format: <size>'<radix> <value>

No of  
bits

Binary	→ b or B
Octal	→ o or O
Decimal	→ d or D
Hexadecimal	→ h or H

Consecutive chars 0-f, x, z
--------------------------------

8'h ax = 1010xxxx

12'o 3zx7 = 011zzzxxx111

# Timescale in Verilog


---

- The `'timescale` declares the time unit and its precision.

`'timescale <time_unit> / <time_precision>`

ex: `'timescale 10 ns / 1 ns`

**delay= 20 ns**

 

`not #2 u1(cbar, c);`

**Delay=20 ns**

`or #2.54 u2(TEMP[1], IN[2], IN[3]);`

**Delay=25 ns**

`and # 3.55 (OUT, TEMP[0], TEMP[1]);`

**Delay=36 ns**

# Data Types


---

- Nets
  - physical connection between devices
- Registers
  - abstract storage devices
- Parameters
  - run-time constants
- *The positions of three data types define whether they are global to a module or local to a particular always statement*
- *By default, net and register are one-bit wide (a scalar)  
not multi-bit wide (a vector)*


 
# Nets

- Connects between structural elements  
`<nettype> <range>? <delay_spec>? <<net_name> <,net_name>*>`
- Must be continuously driven by
  - Continuous assignment
  - Module or gate instantiation
- Default initial value for a wire is “Z”



Net Types	Functionality
wire, tri	for standard interconnection wires (default)
wor, trior	for multiple drivers that are Wire-ORed
wand, triand	for multiple drivers that are Wire-ANDed
triereg	for nets with capacitive storage
tri1	for nets which pull up when not driven
tri0	for nets which pull down when not driven
supply1	for power rails
supply0	for ground rails

**Note: Some of those net types are un-synthesizable (不能電路合成的)**

# Nets (1/2)

---

wire, wand, wor, tri, supply0, supply1


wire k; // single-bit wire

wire [0:31] w1, w2; // Two 32-bit wires

wire w1;

assign w1=a;


assign w1=b; (error)

 

## Method 1:

wand x;


assign x=j; assign x=i;

 

## Method 2:

wor y;

assign y=o; assign y=p;

 

# Nets (2/2)

---

**tri:** all variables that drive the tri must have a value of Z except one (ensured by the designer).


```
module tri-test(out, condition)
input [1:0] condition;  output out;
reg a, b, c;
tri out;
  always@(condition)
  begin
    a=1'bz; b=1'bz; c=1'bz;
    case (condition)
      2'b00: a=1'b1;
      2'b01: b=1'b0;
      2'b10: c=1'b1;
    endcase
  end
assign out=a;  assign out=b; assign out=c;
endmodule
```

**supply0** ➡ wires tied to logic 0 (ground)

**supply1** ➡ wires tied to logic 1 (power)
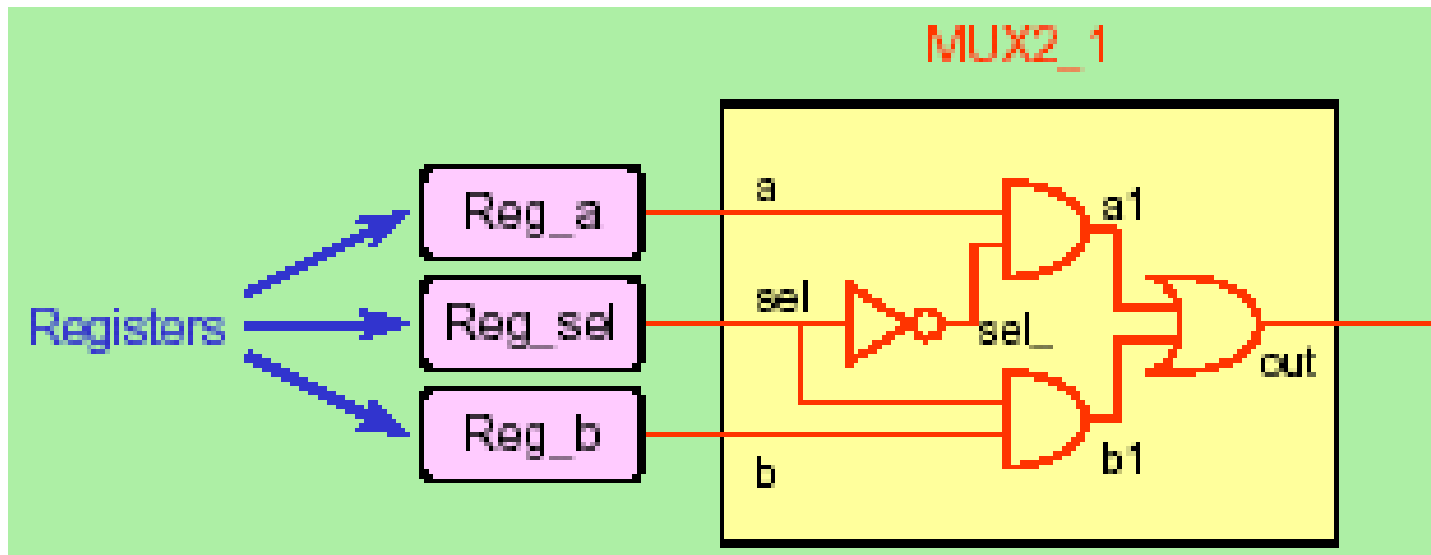
# Registers

- Represent abstract data storage elements
- Hold its value until a new value is assigned to it
- Registers are used extensively in behavioral modeling
- Default initial value for a register is “X”



# Types Of Registers

## ■ Register declaration

<register\_type> <range>? <<register\_name> <,register\_name>\*>

Register Types	Functionality
<b>reg</b>	Unsigned integer variable of varying bit width
<b>integer</b>	Signed integer variable, 32-bit wide. Arithmetic operations producing 2's complement results.
<b>real</b>	Signed floating-point variable, double precision
<b>time</b>	Unsigned integer variable, 64-bit wide

```
reg a;           // a scalar register
reg [3:0] b,c;    // two 4-bit vector registers
reg [7:0] byte_reg; // a 8-bit registers
reg [7:0] memory_block [255:0];
```

***memory-block is an array of 256 registers, each of which is 8 bits width. You can access individual register, but you cannot access individual bits of register directly.***

```
byte_reg=memory_block [120];
bit=byte_reg [7];           // wire bit;
```

# Numbers

- Numbers are integer or real constants. Integer constants are written as `<size>'<base format><number>`
- Real number can be represented in decimal or scientific format.
- A number may be **sized** or **unsized**
- The base format indicates the type of number
  - Decimal (d or D)
  - Hex (h or H)
  - Octal (o or O)
  - Binary (b or B)

Diagram illustrating the components of a number constant:

**unsized example:** `'h72ab`  
The components are: `'` (delimiter), `h` (base format), `72ab` (number).

**sized example:** `16'h72ab`  
The components are: `16` (size), `'` (delimiter), `h` (base format), `72ab` (number).


# Half Adder (1/4)

a\b	0	1
0	0	1
1	1	0

$$\text{sum} = a \oplus b$$

a\b	0	1
0	0	0
1	0	1

$$\text{c\_out} = ab$$

 


## Structural description

```

module Add_half(sum, c_out, a, b);
  input    a, b;
  output   sum, c_out;
  wire     c_out_bar;

  xor      (sum, a, b);
  nand     (c_out_bar, a, b);
  not      (c_out, c_out_bar);
endmodule
  
```

**and** (e, a, b,c,d);

 


# Half Adder (2/4)


## Data flow description

```
module Add_half(sum, c_out, a, b);  
  input    a, b;  
  output   sum, c_out;  
  
  assign   {c_out, sum} = a + b;  
endmodule
```

**assign**: continuous assignment

 

*Synthesized and  
optimized by tools*

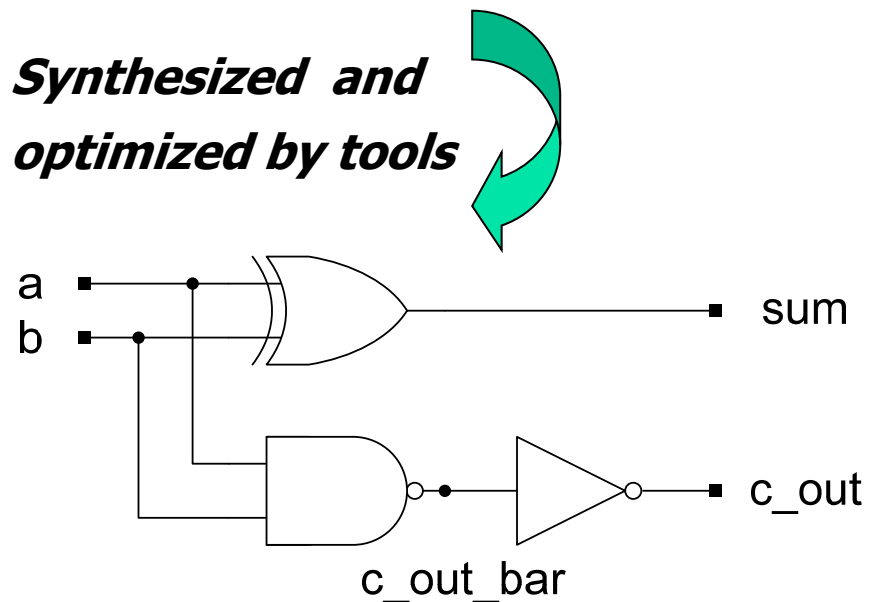





# Half Adder (3/4)
  
## Behavioral description #1

```
module Add_half(sum, c_out, a, b);  
  input    a, b;  
  output   sum, c_out;  
  reg      sum, c_out;
```

```
  always @(a or b)  
  begin  
    sum = a ^ b;  
    c_out = a & b;  
  end  
endmodule
```



# Half Adder (4/4)

## Behavioral description #2

```
module Add_half(sum, c_out, a, b);
input  a, b;
output sum, c_out;
reg    sum, c_out;
always @(a or b)
begin
    case({a,b})
        2'b00:begin
            sum = 0; c_out = 0;
        end
        2'b01:begin
            sum = 1; c_out = 0;
        end
    endcase
end
endmodule
```

```
2'b10:begin
    sum = 1; c_out = 0;
end
default:begin
    sum = 0; c_out = 1;
end
endcase
```

end

endmodule

a\b	0	1	
0	0	1	sum
1	1	0	

a\b	0	1	
0	0	0	c_out
1	0	1	

# Parameter

---

- Parameter declaration

`parameter<range>?<list_of_assignments>`

- You can use a parameter anywhere that you can use a literal.

ex: `module mod(ina, inb,out);`

`.....`

`parameter m1=8;`

`....`

`wire [m1:0] w1;`

`.....`

`endmodule`

w1 can be set as a (n+1)-bit wire if

we change m1 to n

(i.e., m1=10 → w1 becomes a 11-bit wire

m1=4 → w1 becomes a 5-bit wire)

# Parameterized Design

---

```
module PARAM(A , B , C);  
input [7 : 0] A , B;  
output [7 : 0] C;  
wire f;  
    or    o1(f,A,B);  
    test #(4) u1(A , f , C);  
  
endmodule
```

```
module test (a , b , c);  
parameter width = 8;  
input [width - 1 : 0] a, b;  
output [width - 1 : 0] c;  
  
    assign c = a & b;  
  
endmodule
```

**Override the value of width when the test module is instantiated**


**Save the file as PARAM.v and compile (synthesis) it**

 **the width value become 4**

# Expressions

- An expression comprises of **operators** and **operands**, see **Example**, and are covered separately in the following two sections.
- Operands: Four data objects

Example

 

## Verilog Operands

**Identifiers** (mentioned before)

**Literals**

string (bit & character)	4'b 1101
numeric (integer, real <sup>+</sup> )	34

**Function Call**

**Index & Slice Names**

# Identifier and Literal Operands

```
1. module LITERALS(A1, A2, B1, B2, Y1, Y2);  
2.     input  A1, A2, B1, B2;  
3.     output [7:0] Y1; output [5:0] Y2;  
4.     parameter CST = 4'b 1010, TF=25;  
5.     reg [7:0] Y1; reg [5:0] Y2;
```

```
6.     always @(A1 or A2 or B1 or B2)  
7.     begin
```

```
8.         if (A1 == 1)  
9.             Y1 = {CST, 4'b 0000};
```

```
10.        else if (A2 == 1)  
11.            Y1 = {CST, 4'b 0101};
```

```
12.        else  
13.            Y1 = {CST, 4'b 1111};
```

```
14.        if (B1 == 0) Y2 = 10;
```

```
15.        else if (B2 == 1) Y2 = 15;
```

```
16.        else Y2 = TF +10 +15;
```

```
17.     end
```

```
18. endmodule
```

Identifier

Bit string literals

Numeric (integer) literal

Identifier

# Function Call Operands

- Function calls, which must reside in an expression, are **operands**. The **single value returned** from a function is the operand value used in the expression.

```
1.  module FUNCTION_CALLS (A1, A2, A3, A4, B1, B2, B3, B4, Y1, Y2);
2.      input  A1, A2, A3, A4, B1, B2, B3, B4;  output [2:0] Y1, Y2;
3.      reg [2:0] Y1, Y2;

4.      function [2:0] Fn1;
5.          input  F1, F2, F3;
6.          begin
7.              Fn1 = F1+F2+F3;
8.          end
9.      endfunction

10.     always @(A1 or A2 or A3 or A4 or B1 or B2 or B3 or B4)
11.         begin
12.             Y1 = Fn1(A1, A2, A3)+A4;
13.             Y2 = Fn1(B1, B2, B3)-B4;
14.         end
15.     endmodule
```

```
function [2:0] Fn1;
input  F1, F2, F3;
begin
    Fn1 = F1+F2+F3;
end
endfunction
```

Function call operand

# Index and Slice Name Operands (1/2)

---

- **Index operand** specifies a single element of an array and slice operand specifies a sequence of elements within an array


```
1.  module INDEX_SLICE_NAME (A, B, Y);  
2.      input [5:0]      A, B;  
3.      output [11:0]Y;  
4.      parameter      C = 3'b111;  
5.      reg [11:0]      Y;  
  
6.  always @(A or B)  
7.  begin  
8.      Y[2:0]  = A[2:0];  
9.      Y[3]    = A[3] | B[3];  
10.     Y[5:4]  = {A[5] | B[5], A[4] & B[4]};  
11.     Y[8:6]  = B[2:0];  
12.     Y[11:9] = C;  
13. end  
14. endmodule
```



# Index and Slice Name Operands (2/2)

**parameter**       $C = 3'b111$ ;  
 $Y[2:0] = A[2:0];$     $Y[3] = A[3] \mid B[3];$   
 $Y[5:4] = \{A[5] \mid B[5], A[4] \& B[4]\};$   
 $Y[8:6] = B[2:0];$     $Y[11:9] = C;$

A[2:0]	000	010	100	101	110
A[3]	0	1	0	1	0
A[4]	0	1	0	1	0
A[5]	0	1	0	1	0
B[2:0]	110	111	101	001	000
B[3]	0	0	1	1	0
B[4]	0	0	1	1	0
B[5]	0	0	1	1	0
Y[0:2]	000	010	100	101	110
Y[3]	0	1	1	1	0
Y[5:4]	00	10	10	11	00
Y[8:6]	110	111	101	001	000
Y[11:9]	111	111	111	111	111

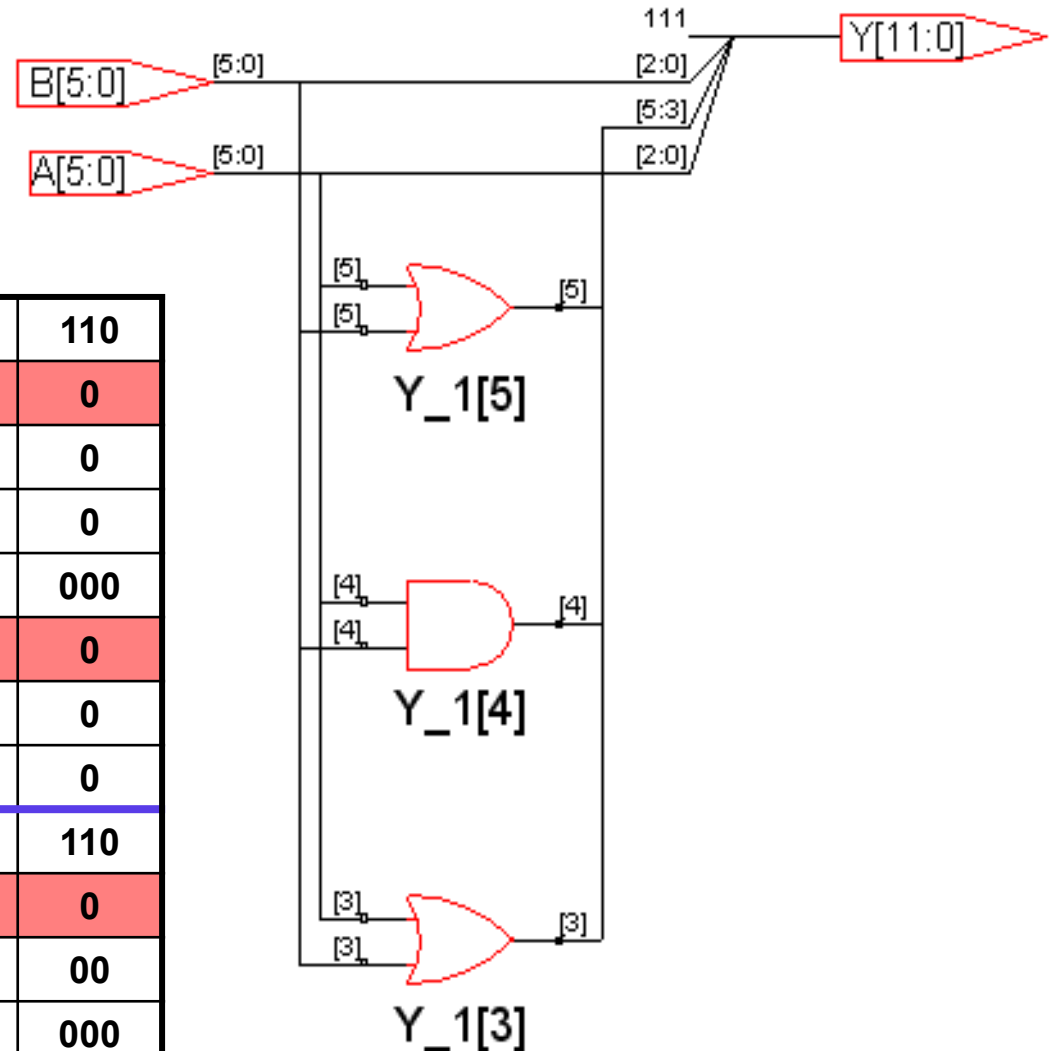

# Operators (1/2)

- **Operators** perform an **operation** on one or more **operands** within an **expression**. An expression combines operands with appropriate operators to produce the desired function expression.

Name	Operator
bit-select or part-select	[ ]
parenthesis	( )
<b>Arithmetic Operators</b>	
multiplication	*
division	/
addition	+
subtraction	-
modulus	%
<b>Sign Operators</b>	
identity	+
negation	-

It is not recommended to use the following three operators:

\*

/ : (not synthesizable)

% : (not synthesizable)

# Operators (2/2)

Name	Operator
<b>Relational Operators</b>	
less than	<
less than or equal to	<=
greater than	>
greater than or equal to	>=
<b>Equality Operators</b>	
logic equality	==
logic inequality	!=
case equality	===
case inequality	!==
<b>Logical Comparison Operators</b>	
NOT	!
AND	&&
OR	
<b>Logical Bit-Wise Operators</b>	
unary negation NOT	~
binary AND	&
binary OR	
binary XOR	^
binary XNOR	^~ or ~^

Name	Operator
<b>Shift Operators</b>	
logical shift left	<<
logical shift right	>>
<b>Concatenation &amp; Replication Operators</b>	
concatenation	{ }
replication	{ { } }
<b>Reduction Operators</b>	
AND	&
OR	
NAND	~&
NOR	~
XOR	^
XNOR	^~ or ~^
<b>Conditional Operator</b>	
conditional	?:

# Relational Operators

```
1. module RELATIONAL_OPERATORS(A, B, Y);
2.     input [2:0]    A;
3.     input [2:0]    B;
4.     output [3:0]   Y;
5.     reg [3:0] Y;

6.     always @(A or B)
7.     begin
8.         Y[0] = A > B;
9.         Y[1] = A >= B;
10.        Y[2] = A < B;
11.        if ( A <= B)
12.            Y[3] = 1;
13.        else
14.            Y[3] = 0;
15.    end
16. endmodule
```

Relational operators:

(1) <

(2) <=

(3) >=

(4) >

A[2:0]	1	2	3	4	5	6	7	3	0
B[2:0]	3	5	6	7	2	1	0	3	6
Y[3]	1	1	1	1	0	0	0	1	1
Y[2]	1	1	1	1	0	0	0	0	1
Y[1]	0	0	0	0	1	1	1	1	0
Y[0]	0	0	0	0	1	1	1	0	0

# Equality & Inequality Operators

```
1. module EQUALITY_OPERATORS(A, B, Y);
2.     input [2:0]      A;
3.     input [2:0]      B;
4.     output [4:0]     Y;
5.     reg [4:0] Y;

6.     always @(A or B)
7.     begin
8.         Y[0] = A != B;
9.         Y[1] = A == B;
10.        if ( A == B)
11.            Y[4:2] = A;
12.        else
13.            Y[4:2] = B;
14.    end

15. endmodule
```

Equality operators:

- (1) == (等於)
- (2) != (不等於)
- (3) === (++) non-syn.
- (4) !== (++) non-syn.

When comparison is true, the result is 1

When comparison is false, the result is 0

A[2:0]	0	7	4	1	0
B[2:0]	3	7	3	4	5
Y[0]	1	0	1	1	1
Y[1]	0	1	0	0	0
Y[4:2]	3	7	3	4	5

# Logical Bit-Wise Operators

```
module BITWISE(A, B, Y1, Y2, Y3, Y4, Y5);
```

```
    input [3:0]  A;
```

```
    input [3:0]  B;
```

```
    output [3:0] Y1, Y2, Y3, Y4, Y5;
```

```
    reg [3:0]    Y1, Y2, Y3, Y4, Y5;
```

```
always @(A or B)
```

```
begin
```

```
    Y1 = ~A;
```

```
    Y2 = A & B;
```

```
    Y3 = A | B;
```

```
    Y4 = A ^ B;
```

```
    Y5 = A ^ ~B;
```

```
end
```

```
endmodule
```

Logic bit-wise operators:

(1) ~ (unary NOT)

(2) & (binary AND)

(3) | (binary OR)

(4) ^ (binary XOR)

(5) ^~ or ~^ (binary XNOR)

```
    0110
    & 0011
    ---
    0010

    0110
    | 0011
    ---
    0111
```

A[3:0]	0000	0001	0010	0110
B[3:0]	0000	0000	0001	0011
Y1[3:0]	1111	1110	1101	1001
Y2[3:0]	0000	0000	0000	0010
Y3[3:0]	0000	0001	0011	0111
Y4[3:0]	0000	0001	0011	0101
Y5[3:0]	1111	1110	1100	1010

# Concatenation & Replication Operators

```

1.  module CONCATENATION (A, B, Y);
2.      input [2:0]      A;
3.      input [2:0]      B;
4.      output [14:0]    Y;

5.      reg [14:0]       Y;

6.      parameter        C=3'b011;

7.      always @(A)
8.      begin
9.          Y = { B, A, { 2 { C } }, 3'b 001};
10.     end
11. endmodule

```

Concatenation    { }

Replication      { { } }

A[2:0]	000	001	010	011
B[2:0]	000	010	100	110
Y[14:0]	000	010	100	110
	000	001	010	011
	<u>011</u>	<u>011</u>	<u>011</u>	<u>011</u>
	<u>011</u>	<u>011</u>	<u>011</u>	<u>011</u>
	001	001	001	001

$$3+3+2*3+3=15$$

# Reduction Operators

```

module REDUCTION (A, Y);
    input [3:0] A;
    output [5:0] Y;

    reg [5:0] Y;
  
```

```

always @(A)
begin
  Y[0] = & A;
  Y[1] = | A;
  Y[2] = ~& A;
  Y[3] = ~| A;
  Y[4] = ^ A; // XOR, 奇同位
  Y[5] = ~^ A; //XNOR, 偶同位
end
endmodule
  
```

Reduction operators:

(1) &    (2) |  
 (3) ~&   (4) ~|  
 (5) ^    (6) ~^

$\& A \Rightarrow A[0] \& A[1] \& A[2] \& A[3]$

$| A \Rightarrow A[0] | A[1] | A[2] | A[3]$

$\wedge A \Rightarrow A[0] \wedge A[1] \wedge A[2] \wedge A[3]$

A[3]	0	0	0	0
A[2]	0	0	0	0
A[1]	0	0	1	1
A[0]	0	1	0	1
Y[5:0]	101100	010110	010110	100110



# Conditional Operators

```

1.  module ADD_SUB (A, B, SEL, Y);
2.  input [7:0] A;  input [7:0] B;
3.  input          SEL;
4.  output [8:0]    Y1,Y2;
5.  reg [8:0]  Y2,Y1;
6.  always @( A or B)
7.  begin
8.    Y1 = ( SEL == 1 ) ? A + B : A - B ;
9.    Y2 = (!SEL) ? A : B;
10. end

```


Conditional operators:  
? :

SEL	0	0	1	1
A[7:0]	00000100	00000001	00000100	00000001
B[7:0]	00000001	00000010	00000001	00000010
Y1[8:0]	00000011	11111111	00000101	00000011
Y2[8:0]	00000100	00000001	00000001	00000010
 
# Array of Instances

```
module array_of_nor(y, a, b);  
  input      [0:7] a, b;  
  output     [0:7] y;  
  
  nor        (y[0], a[0], b[0]);  
  nor        (y[1], a[1], b[1]);  
  nor        (y[2], a[2], b[2]);  
  nor        (y[3], a[3], b[3]);  
  nor        (y[4], a[4], b[4]);  
  nor        (y[5], a[5], b[5]);  
  nor        (y[6], a[6], b[6]);  
  nor        (y[7], a[7], b[7]);  
endmodule
```

```
module array_of_nor(y, a, b);  
  input      [0:7] a, b;  
  output     [0:7] y;  
  
  nor        [0:7] (y, a, b);  
endmodule
```



8-bit NOR array

# Two alternatives for Continuous Assignment

```
module bit_or8_gate1(y, a, b);
```

```
    input      [7:0] a, b;  
    output    [7:0] y;
```



```
    assign     y = a | b;  
endmodule
```

```
module bit_or8_gate2(y, a, b);
```

```
    input      [7:0] a, b;
```

```
    output    [7:0] y;
```

```
    wire      [7:0] y = a | b;  
endmodule
```

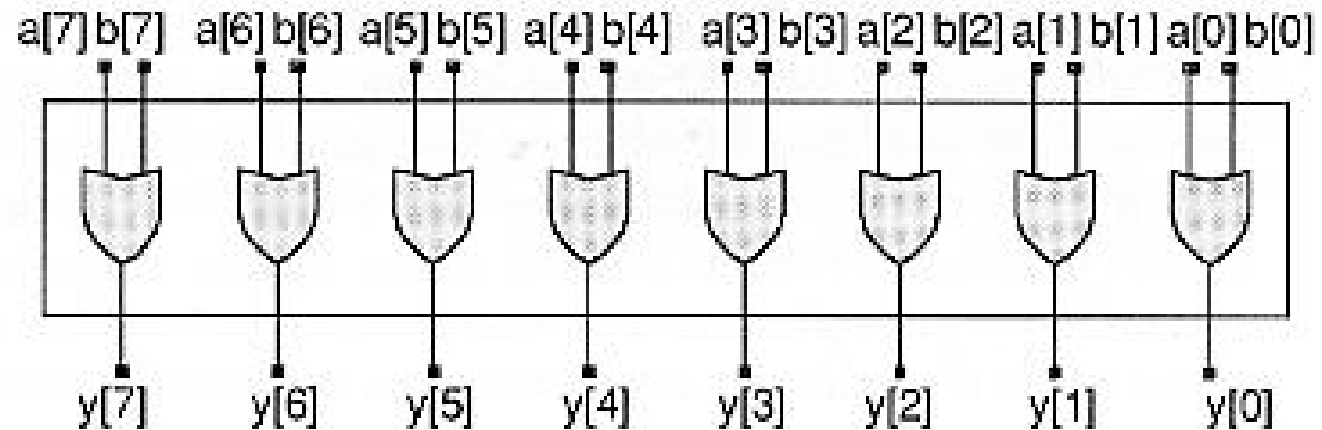 

# Multiple Instantiations and Assignments

---

```
module Multiple_Gates(y1, y2, y3, a1, a2, a3, a4);  
  input      a1, a2, a3, a4;  
  output     y1, y2, y3;
```


```
nand #1 G1(y1, a1, a2, a3), (y2, a2, a3, a4), (y3, a1, a4);  
endmodule
```

```
module Multiple_Assigns(y1, y2, y3, a1, a2, a3, a4);  
  input      a1, a2, a3, a4;  
  output     y1, y2, y3;
```

```
  assign #1   y1 = a1 ^ a2, y2 = a2 | a3, y3 = a1 + a2;  
endmodule
```


# 3 to 8 Decoder (1/4)

---

 

E	In[2]	In[1]	In[0]	Out[7]	Out[6]	Out[5]	Out[4]	Out[3]	Out[2]	Out[1]	Out[0]
0	X	X	X	0	0	0	0	0	0	0	0
1	0	0	0	0	0	0	0	0	0	0	1
1	0	0	1	0	0	0	0	0	0	1	0
1	0	1	0	0	0	0	0	0	1	0	0
1	0	1	1	0	0	0	0	1	0	0	0
1	1	0	0	0	0	0	1	0	0	0	0
1	1	0	1	0	0	1	0	0	0	0	0
1	1	1	0	0	1	0	0	0	0	0	0
1	1	1	1	1	0	0	0	0	0	0	0

# 3 to 8 Decoder (2/4)

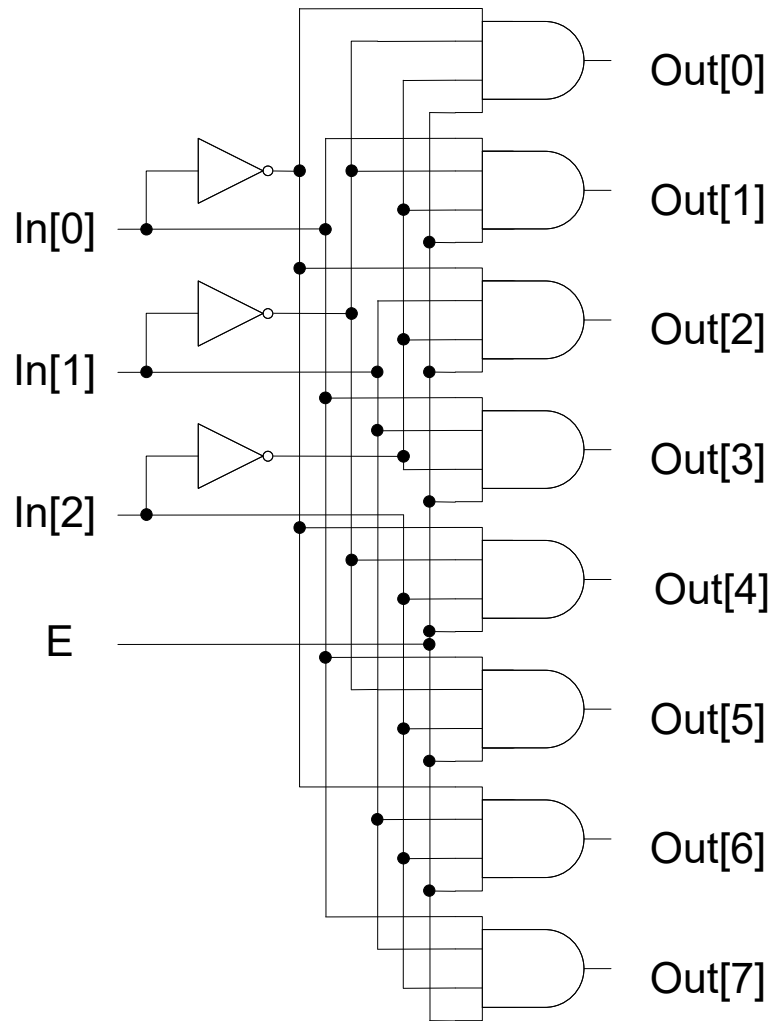

## Structural description

```
1.  module decoder (E , In , Out);
2.  input E;  input [2:0] In;
3.  output [7:0] Out;
4.  wire [7:0] Out;
5.  wire tmp0 , tmp1 , tmp2;

6.  not not1(tmp0,In[0]); not not2(tmp1,In[1]);
7.  not not3(tmp2,In[2]);
8.  and and0(Out[0] , E , tmp0 , tmp1 , tmp2);
9.  and and1(Out[1] , E , In[0] , tmp1 , tmp2);
10. and and2(Out[2] , E , tmp0 , In[1] , tmp2);
11. and and3(Out[3] , E , In[0] , In[1] , tmp2);
12. and and4(Out[4] , E , tmp0 , tmp1 , In[2]);
13. and and5(Out[5] , E , In[0] , tmp1 , In[2]);
14. and and6(Out[6] , E , tmp0 , In[1] , In[2]);
15. and and7(Out[7] , E , In[0] , In[1] , In[2]);
16. endmodule
```

\_\_\_\_\_

1	2	3	465	466
---	---	---	---	---	---	---	---	---	----	----	----	----	-----	-----	-----	-----	-----

\_\_\_\_\_

\_\_\_\_\_

[illegible]

Journal of Management Inquiry 24(1) 1-14

[illegible]

**THE**

# 3 to 8 Decoder (4/4)

## Behavioral description

```
module Decoder_Behavioral(E, In, Out);  
    Input          E;  
    input  [2:0]    In;  
    output [7:0]    Out;  
    reg   [7:0]    Out;  
    always @(E or In)  
    begin  
        if(!E)  
            Out = 8'h00;  
        else  
            begin  
                case(In)  
                    3'b000: Out = 8'h01;  
                    3'b001: Out = 8'h02;  
                    3'b010: Out = 8'h04;  
                    3'b011: Out = 8'h08;
```


```
                    3'b100: Out = 8'h10;  
                    3'b101: Out = 8'h20;  
                    3'b110: Out = 8'h40;  
                    default: Out = 8'h80;  
                endcase
```

```
            end
```

```
        end
```

```
    endmodule
```

E	In			Out							
0	X	X	X	0	0	0	0	0	0	0	0
1	0	0	0	0	0	0	0	0	0	0	1
1	0	0	1	0	0	0	0	0	0	1	0
1	0	1	0	0	0	0	0	1	0	0	0
1	0	1	1	0	0	0	0	1	0	0	0
1	1	0	0	0	0	0	1	0	0	0	0
1	1	0	1	0	0	1	0	0	0	0	0
1	1	1	0	0	1	0	0	0	0	0	0
1	1	1	1	1	0	0	0	0	0	0	0

 



# Hierarchical Design of 3-8 decoder

```

module decoder_2_4(E , In , Out);
input E;      input [1:0] In;
output [3:0] Out;  wire [3:0] Out;


assign Out = E ? 1'b1 << In : 4'h0;

endmodule
2 to 4 decoder
    
```

```


module decode_3_8(E , In , Out);
input E;      input [2:0] In;
output [7:0] Out;  wire E1 , G1 , G2;

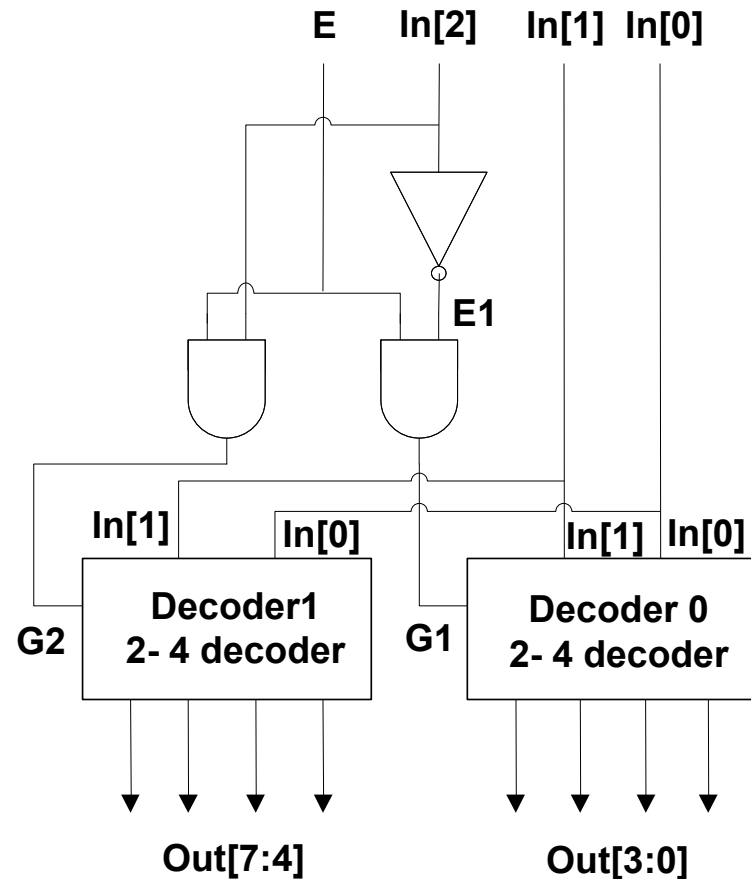    not u1(E1 , In[2]); and a1(G1 , E , In[2]);
    and a2(G2 , E , E1);
    decoder_2_4 M(G1 , In[1 : 0] , Out[7 : 4]);
    decoder_2_4 L(G2 , In[1 : 0] , Out[3 : 0]);
endmodule
    
```



# Simulation

---

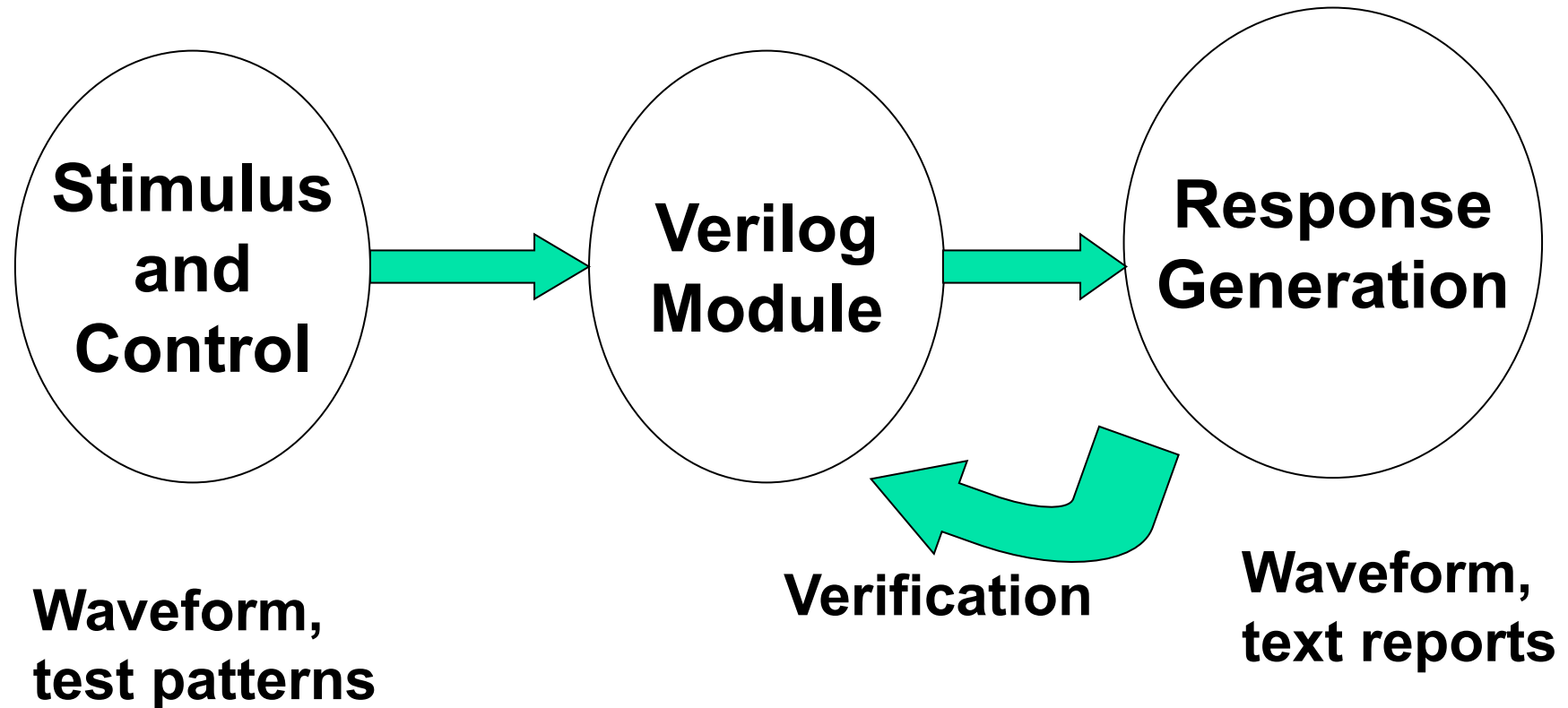

**Test Bench**

# ModelSim Test\_Bench Simulation (1/4)

---

## Test\_bench

```
module or_and_tb;
reg in1, in2, in3, in4;
wire out;
or_and ok(.in1(in1), .in2(in2),
          .in3(in3), .in4(in4), .out(out
          ));
initial
begin
#0   in1=0; in2=0; in3=0; in4=0;
#10  in1=0; in2=0; in3=0; in4=1;
#10  in1=0; in2=0; in3=1; in4=0;
#10  in1=0; in2=0; in3=1; in4=1;
#10  in1=0; in2=1; in3=0; in4=0;
#10  in1=0; in2=1; in3=0; in4=1;
#10  in1=0; in2=1; in3=1; in4=0;
#10  in1=0; in2=1; in3=1; in4=1;
```


```
#10 in1 = 1; in2 = 0; in3 = 0; in4 = 0;
#10 in1 = 1; in2 = 0; in3 = 0; in4 = 1;
#10 in1 = 1; in2 = 0; in3 = 1; in4 = 0;
#10 in1 = 1; in2 = 0; in3 = 1; in4 = 1;
#10 in1 = 1; in2 = 1; in3 = 0; in4 = 0;
#10 in1 = 1; in2 = 1; in3 = 0; in4 = 1;
#10 in1 = 1; in2 = 1; in3 = 1; in4 = 0;
#10 in1 = 1; in2 = 1; in3 = 1; in4 = 1;
```

```
end
```

```
endmodule
```
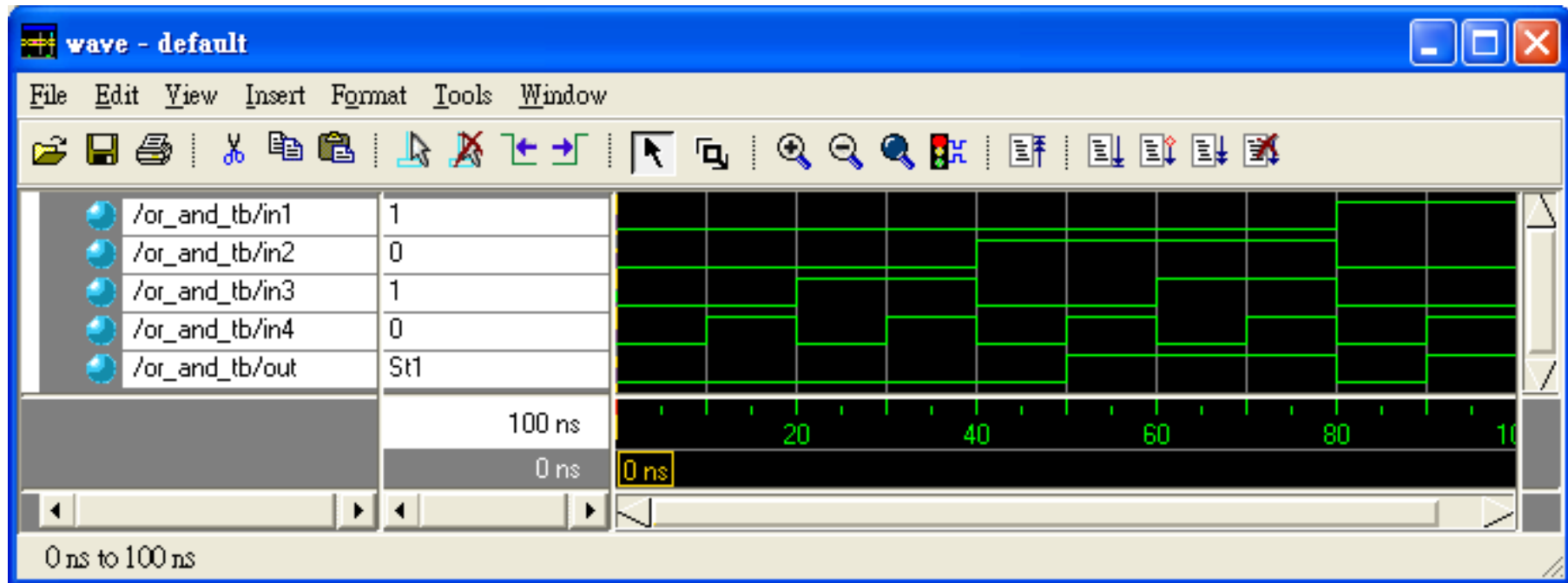
# ModelSim Test\_Bench Simulation (2/4)

Functional simulation only (no delay is introduced)



In ModelSim, Input: test patterns (using comds.)    Output: waveform

In Altera,    Input: waveform    Output: waveform

# ModelSim Test\_Bench Simulation (3/4)

---

## Test\_bench

```
module decoder_3_8_tb;

    reg      E;
    reg [2:0] in;

    wire [7:0] out;

    decoder
        ok(.E(E), .in(in), .out(out));

    initial
    begin


        #0  E = 0; in = 3'b000;
        #10 E = 1; in = 3'b000;
        #10 E = 1; in = 3'b001;
        #10 E = 1; in = 3'b010;
        #10 E = 1; in = 3'b011;
        #10 E = 1; in = 3'b100;
        #10 E = 1; in = 3'b101;
        #10 E = 1; in = 3'b110;
        #10 E = 1; in = 3'b111;

        end
    endmodule
```

***Exhaustive test or partial test for functional simulation in***

***test\_bench ? How about chip test ? Exhaustive or partial testing?***

# ModelSim Test\_Bench Simulation (4/4)

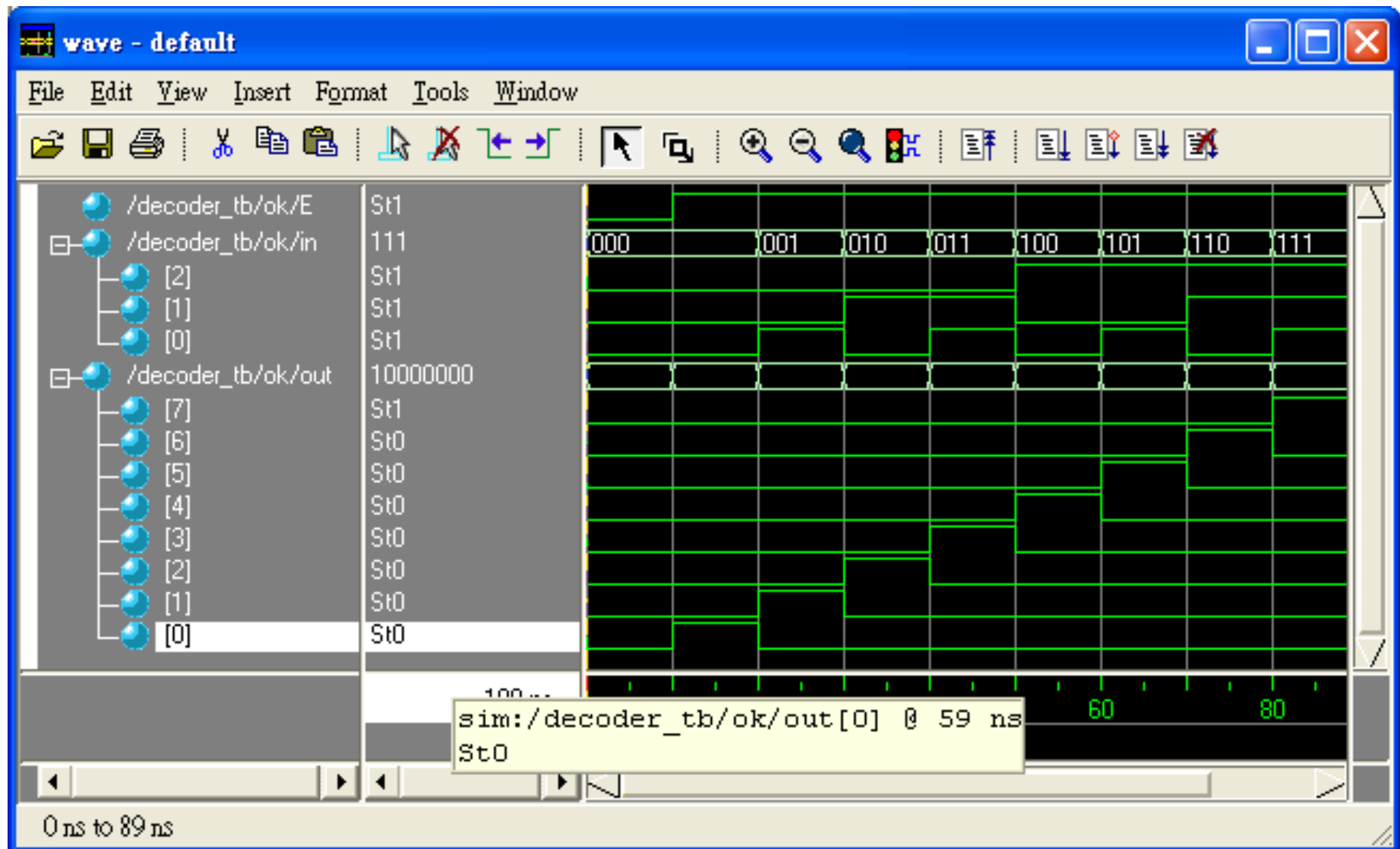

# Begin\_End Statements

---

## Begin-end block statements:

1. Block statements is a way of syntactically grouping several statements into a single statement.
2. Sequential blocks are delimited by the keywords **begin** and **end**. These begin...end pairs are commonly used in conjunction with if, case, and for statements to group several statements.
3. **Functions** and **always** blocks that contain more than one statement require a begin...end pair to group the statements.
4. Verilog provides a construct called a **named** block.

```
begin [: block_name  
  
    reg local_variable_1 ;  
  
    integer local_variable_2 ;  
  
    parameter local_variable_3 ;]  
  
    . . . statements . . .  
  
end
```

Verilog allows you to declare variables (reg, integer and parameter) locally within a named block but not in an unnamed block.

# Named Block (1/2)

---

```
module UNNAMED_BLOCK(A , B , E , Y);
parameter FI = 12;
input [3 : 0]A;
input [3 : 0]B;
input E;
output [4 : 0]Y;

reg [4 : 0]Y;

always @(A or B or E)
begin
    if(E)
        Y = (A + B) & FI;
    else
        Y = (A - B) & FI;
end
endmodule
```

```
module NAMED_BLOCK(A , B , E , Y);
input [3 : 0]A; input [3 : 0]B;
input E; output [4 : 0]Y; reg [4 : 0] Y;

always @(A or B or E)
begin
    if(E)
        begin: Add_And
            parameter FI = 12; // in a named block
            Y = (A + B) & FI;
        end
    else
        begin: Sub_And
            parameter FII = 2; // in a named block
            Y = (A - B) & FII;
        end
    end
end
endmodule
```




# Named Block (2/2)

```
module NAMED_BLOCK(A , B , E , Y);  
input [3 : 0]A; input [3 : 0]B;  
input E;    output [4 : 0]Y;  
reg [4 : 0]Y;
```

```
parameter FI = 1;  
parameter FII = 8;  
always @(A or B or E)  
begin
```

```
if(E)  
begin: Add_And  
    parameter FI = 12;  
    Y = (A + B) + FI; //FI is 12 not 1  
end  
else  
begin: Sub_And  
    parameter FII = 2;  
    Y = (A + B) + FII; //FII is 2 not 8  
end end
```
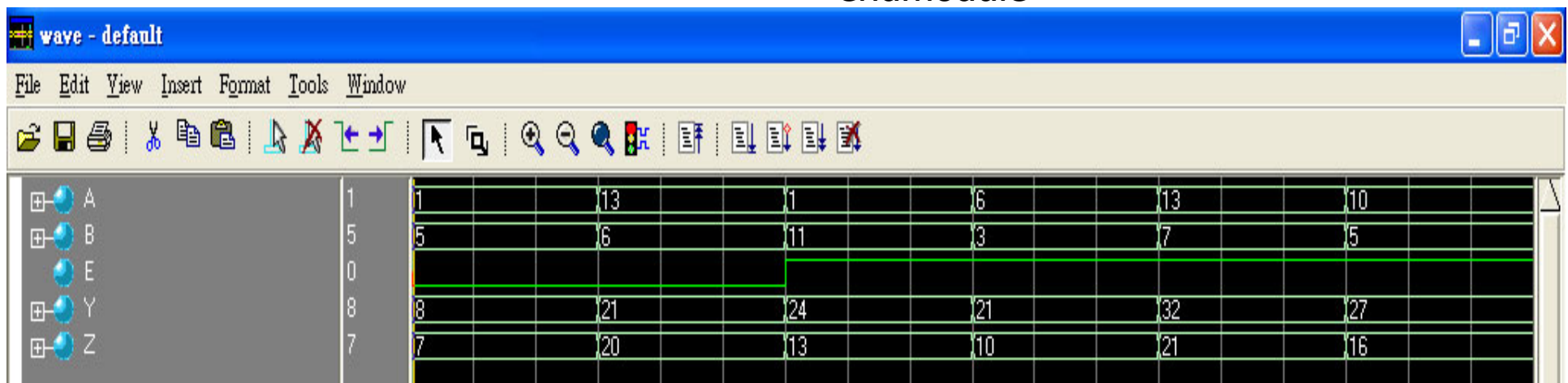
```
assign Z = (A + B) + FI; //FI is 1  
endmodule
```




# If-Else Statements (1/4)

 1. The if statement is followed by a statement or block of statements enclosed by begin and end.
2. If the value of the expression is nonzero, the expression is true and the statement block that follows is executed. If the value of the expression is zero, the expression is false and the statement block following else is executed.
3. If..else statements can cause synthesis of latches.

```
If (expression)
begin
... statements ...
end
[else
begin
... statements ...
end]
```

```
module IF_ELSE(IN1 , IN2 , E , OUT);
input IN1, IN2, E;
output [1 : 0] OUT;  reg [1 : 0]OUT;
always @(IN1 or IN2 or E)
begin
    if(E == 1)
        OUT = IN1 + IN2;
    else
        OUT = IN1;    end
endmodule
```




# If-Else Statements (2/4)

```
Module Latch(In, Enable, Out);  
input      Enable;  
Input  [3:0] In;  
output [3:0] Out;  
always @(In or Enable)  
begin  
    if(Enable)  
        Out=In;  
    else  
        Out=0;  
    end  
end  
endmodule
```

No latch inference

 
```
Always@ (In or  
Enable)  
begin  
    Out=0;  
    if(Enable)  
        Out=In;  
end // no latch
```


 
## Watch for unintentional Latches

```
Module Latch(In, Enable, Out);  
input      Enable;  
input  [3:0] In;  
output [3:0] Out;  
  
always @(In or Enable)  
begin  
    if(Enable)  
        Out=In;  
    end  
end  
endmodule
```

If Enable == 1  
Out (new) = In  
If Enable == 0  
Out (new) = Out (old)



# If-Else Statements (3/4)

```

module IF_ELSE_VALUE(IN , OUT);
input [1 : 0]IN;
output [1 : 0]OUT;
reg [1 : 0]OUT;
always @(IN)
begin
    if(IN==1)
        OUT = 2'b00;
    else
        OUT = 2'b11;
end
endmodule

```

IN=0,OUT=11  
IN=1,OUT=00  
IN=2,OUT=11  
IN=3,OUT=11

OUT = 2'b00; true  
OUT = 2'b11; false

```


module IF_ELSE_VALUE(IN , OUT);
input [1 : 0]IN;
output [1 : 0]OUT;
reg [1 : 0]OUT;
always @(IN)
begin
    if(IN)
        OUT = 2'b00;
    else
        OUT = 2'b11;
end
endmodule

```

IN=0,OUT=11  
IN=1,OUT=00  
IN=2,OUT=00  
IN=3,OUT=00

OUT = 2'b00; nonzero ⇒ true  
OUT = 2'b11; zero ⇒ false


What is the difference between them?

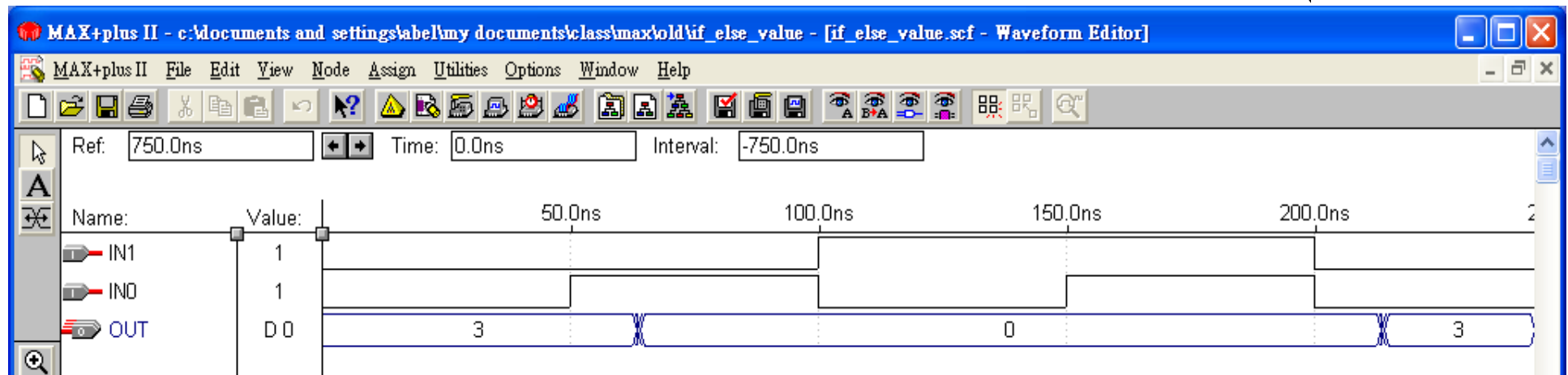
 
# If-Else Statements (4/4)

*if-then-else* statement implies priority-encoded MUXs

```
always @(sel or a or b or c or d)
  if (sel[2] == 1'b1)
    out = a;    //sel=1XX
  else if (sel[1] == 1'b1)
    out = b;    //sel=01X
  else if (sel[0] == 1'b1)
    out = c;    //sel=001
  else
    out = d;    //sel=000
```




# Resource Sharing (1/2)

- Assign similar operations to a common netlist cell
  - reduce hardware
  - may degrade performance
  - resource sharing within the same **always block**
  - resource sharing **not done** for **conditional operator**

## Without resource sharing


```
assign z = sel_a ? a+t : b+t;
```

 

Hence, in this case you better use if statement not conditional operator "?" to save a lot of cost and area
 
## Resource sharing

```
if (sel_a)  
    z = a + t;  
else  
    z = b + t;
```



# Resource Sharing (2/2)

```
module noshare(v, w, x, z, k);  
input [2:0]k,v,w;  
input x;  
output [3:0]z;  
wire [3:0]y;  
  
assign y=x?k+w:k+v;  
assign z=x?y+w:y+v;  
  
endmodule
```



Without resource sharing

With resource sharing



```
module share(v, w, z,k);  
input [2:0] k,v,w;  
input x; output [3:0]z;  
reg [3:0] y,z;  
  
always@(x or k or v or w)  
begin  
    if(x)  
        y=k+w;  
    else  
        y=k+v;  
end  
always@(y or x or w or v)  
begin  
    if(x)  
        z=y+w;  
    else  
        z=y+v;  
end  
endmodule
```

# Case Statements (1/4)

The case statement consists of the keyword case, followed by an expression in parentheses, followed by one or more case items (and associated statements to be executed), followed by the keyword endcase. A case item consists of an expression (usually a simple constant) or a list of expressions separated by commas, followed by a colon (:).

```
module FULL_CASE(IN , OUT);  
input  [1 : 0]IN;output [3 : 0] OUT;  
reg [3 : 0]OUT;  
always @(IN)  
begin  
    case(IN)  
        2'b00: OUT = 4'b0001;  
        2'b01: OUT = 4'b0010;  
        2'b10: OUT = 4'b0100;  
        2'b11: OUT = 4'b1000;  
    endcase  
end  
endmodule
```

```
module FULL_CASE(IN , OUT);  
input  [1 : 0]IN;output [3 : 0] OUT;  
reg [3 : 0]OUT;  
always @(IN)  
begin  
    case(IN)  
        2'b00: OUT = 4'b0001;  
        2'b01: OUT = 4'b0010;  
        2'b10: OUT = 4'b0100;  
    endcase // not full-case, latches are inferred  
end  
endmodule
```


case (expression)

```
case_item 1:  
    begin  
        . statements .  
    end  
case_item 2:  
    begin  
        . statements .  
    end  
...  
default:  
    begin  
        . statements .  
    end  
endcase
```


 
# Case Statements (2/4)

If the conditional expression used is mutually exclusive (i.e. parallel) and the functional outputs are the same, then the hardware synthesized will be same.



```
always @ (sel or a or b or c or d)
begin
    case (sel)
        2'b00: out = a;
        2'b01: out = b;
        2'b10: out = c;
        default : out = d;
    endcase
end
```

```
always @(sel or a or b or c or d)
if (sel == 2'b00)
    out = a;
else if (sel == 2'b01)
    out = b;
else if (sel == 2'b10)
    out = c;
else
    out = d;
```

# Case Statements (3/4)

---

```
module FULL_CASE(IN , OUT);
input [1 : 0]IN; output [3 : 0] OUT;
reg [3 : 0]OUT;
always @(IN)
begin
    case(IN)
        2'b00: OUT = 4'b0001;
        2'b01: OUT = 4'b0010;
        2'b10: OUT = 4'b0100;
        2'b11: OUT = 4'b1000;
    endcase
end
endmodule
```


```
module FULL_CASE(IN , OUT);
input [1 : 0]IN; output [3 : 0] OUT;
reg [3 : 0]OUT;
always @(IN)
begin
    case(IN)
        2'b00: OUT = 4'b0001;
        2'b01: OUT = 4'b0010;
        2'b10: OUT = 4'b0100;
        default: OUT = 4'b1000;
    endcase
end
endmodule
```

It is always a good idea to use default-case-item in all conditions to make sure no latch is inferred.

# Case Statements (4/4)
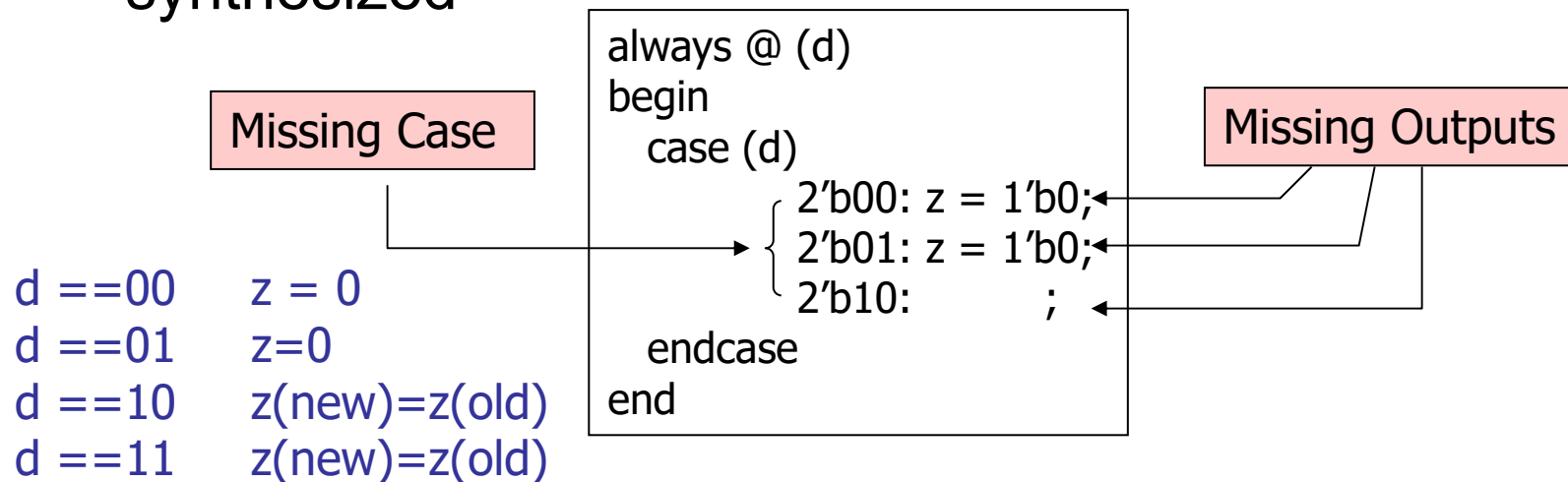
## Watch Out for Unintentional Latches

- Completely specify all clauses for every **case** and **if** statement
- Completely specify all output for every clause of each **case** or **if** statement
- Failure to do so will cause latches or flip-flops to be synthesized



# Casez and Casex Statements

---

casez (expression)

```
case_item 1:
  begin
    . statements . .
  end
case_item 2:
  begin
    . statements. .
  end
. . . . .
default:
  begin
    . statements. .
  end
endcase
```

casez:

The case item  
can use z or ?

casex:

The case item  
can use z, x,  
or ?


casex (expression)

```
case_item 1:
  begin
    . statements . .
  end
case_item 2:
  begin
    . statements. .
  end
. . . . .
default:
  begin
    . statements. .
  end
endcase
```

casez is one of the conditions in casex
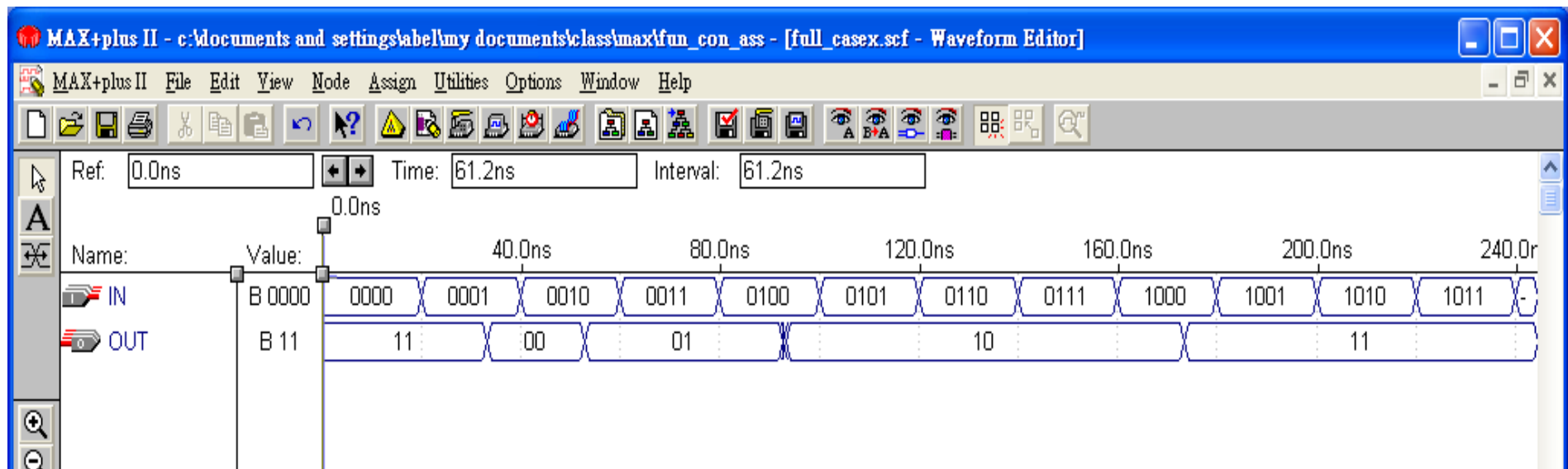
# Case Statement

```
module FULL_CASEX(IN , OUT);  
  input [3 : 0] IN;  
  output [1 : 0] OUT;  
  
  reg [1 : 0] OUT;  
  
  always @(IN)  
  begin  
    casex(IN)  
      4'b0001: OUT = 2'b00;  
      4'b001?: OUT = 2'b01;  
      4'b01??: OUT = 2'b10;  
      default: OUT = 2'b11;  
    endcase  
  end  
endmodule
```



# For Loop Statements (1/2)

---

The for loop repeatedly executes a single statement or block of statements. The repetitions are performed over a range determined by the range expressions assigned to an index. Two range expressions appear in each for loop: low\_range and high\_range. In the syntax lines that follow, high\_range is greater than or equal to low\_range. HDL Compiler recognizes incrementing as well as decrementing loops. The statement to be duplicated is surrounded by begin and end statements.

```
for (index = low_range; index < high_range; index = index + step)
for (index = high_range; index > low_range; index = index - step)
for (index = low_range; index <= high_range; index = index + step)
for (index = high_range; index >= low_range; index = index - step)
```

```
for (i = 0; i <= 31; i = i + 1)
```

```
begin
```

For statement: unrolling the logic

```
    s[i] = a[i] ^ b[i] ^ carry;
```

```
    carry = (a[i] & b[i]) | (a[i] & carry) | (b[i] & carry);
```

```
end
```

# For Loop Statements (2/2)

*for* loop are “unrolled”, and then synthesized.


```
integer i;  
always @(a r b)  
begin  
    for (i = 0; i < 6; i = i+1)  
        example[i] <= a[i] & b[5-i];  
end
```

**Verilog for loop**



```
example [0] <= a[0] and b[5];  
example [1] <= a[1] and b[4];  
example [2] <= a[2] and b[3];  
example [3] <= a[3] and b[2];  
example [4] <= a[4] and b[1];  
example [5] <= a[5] and b[0];
```

**for loop unrolled**

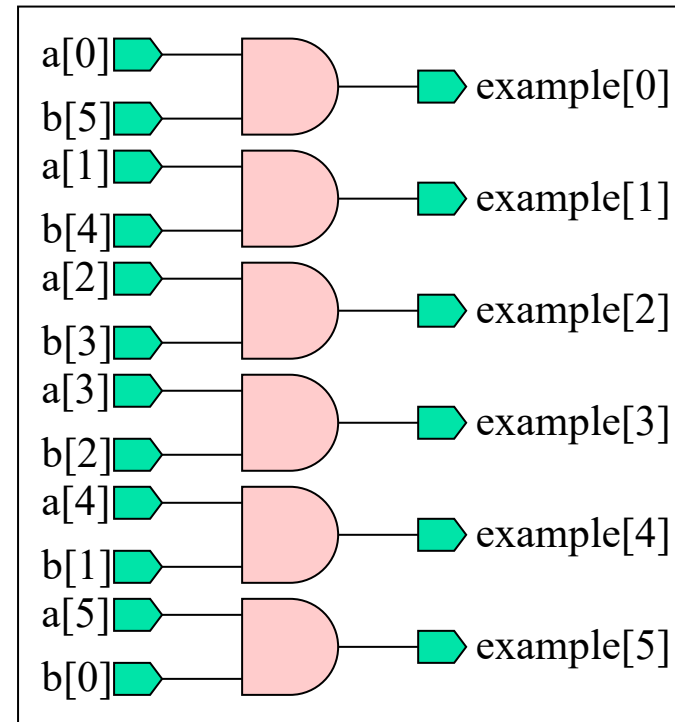

**for loop synthesized to gates**

# Sorting Problem (1/2)

Bubble Sort: (four inputs)

1. (0)?(1) (compare temp[0] and temp [1],  
then the bigger value is stored in temp[1])  
(1)?(2) (compare temp[1] and temp [2],...)  
(2)?(3) (compare temp[2] and temp [3],...)
2. (0)?(1), (1)?(2)
3. (0)?(1)


Totally, six comparators are needed  
for parallel comparisons of 4 inputs

```
module for_loop(a,b,c,d,out);  
input [3:0]a,b,c,d;  
output [3:0]out;  
reg [3:0] temp [3:0];  
reg [3:0] buffer,out;  
integer i,j;
```

```
always@(a or b or c or d)  
begin  
    temp[0]=a;  
    temp[1]=b;  
    temp[2]=c;  
    temp[3]=d;  
    for(i=2;i>=0;i=i-1)  
        for(j=0;j<=i;j=j+1)  
            if(temp[j]>temp[j+1])  
                begin  
                    buffer=temp[j+1];  
                    temp[j+1]=temp[j];  
                    temp[j]=buffer;  
                end  
        out=temp[3];  
    end  
endmodule
```



# Sorting Problem (2/2)

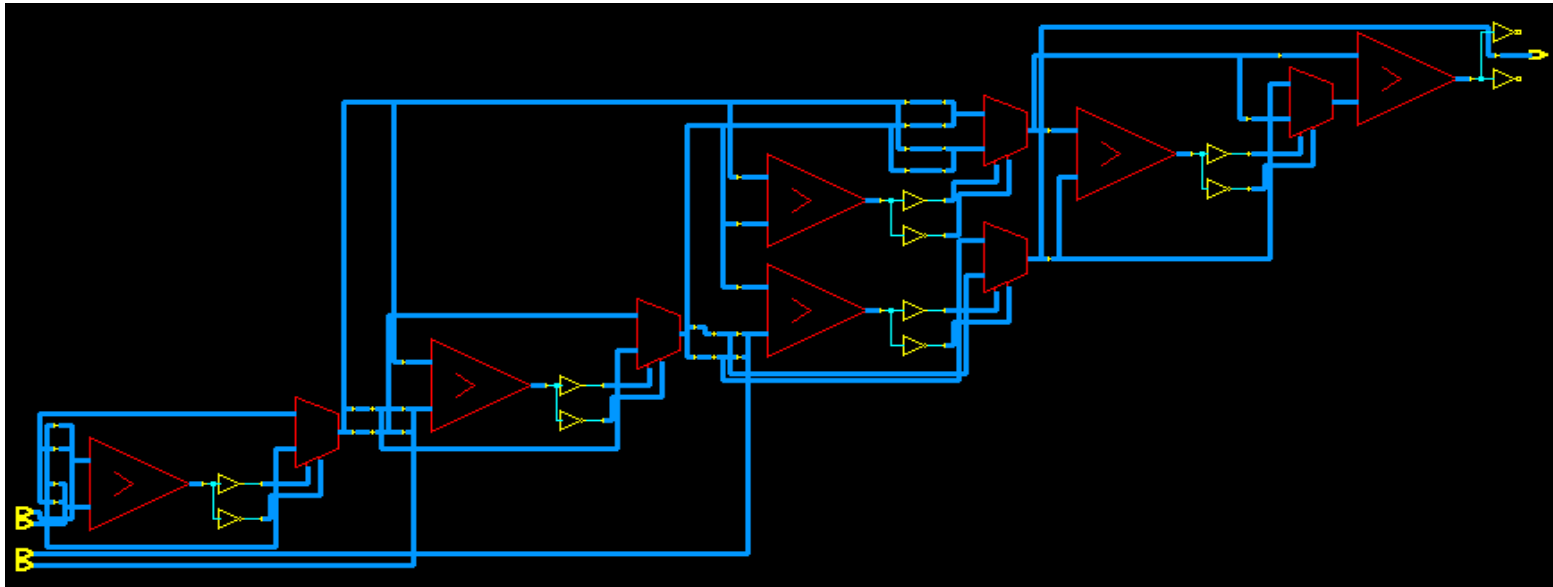

Bubble Sort: (four inputs)

(0)?(1), (1)?(2), (2)?(3)

(0)?(1), (1)?(2)

(0)?(1)      critical path=6.01 ns

Totally, 6 comparators are needed  
for parallel comparisons

Bubble Sort: (five inputs)

(0)?(1), (1)?(2), (2)?(3), (3)?(4)

(0)?(1), (1)?(2), (2)?(3)

(0)?(1), (1)?(2)

(0)?(1)      critical path=8.05 ns

Totally, 10 comparators are needed

The more inputs, the longer delay → use one comparator and a suitable FSM

# Always Block (1/3)

An always block can imply latches or flip-flops, or it can specify purely combinational logic. An always block can contain logic triggered in response to a change in a level (asynchronous triggers) or the rising or falling edge of a signal (synchronous triggers).

The syntax of an always block is

```
always @ (event-expression )
```

```
begin
```

```
... statements ...
```

```
end (combinational circuit)
```

Completely specify sensitivity lists to avoid error

x is recalculated as soon as any input (a or b or c) has a level transition (0 to 1 or 1 to 0).

## Asynchronous triggers

```
always@ (a or b or c)
```


```
begin
```

```
x=a | b | c;
```

```
end
```
 
# Always Block (2/3)

```
always @ ( [posedge or negedge] event)
begin
    . . . statements . . .
end (sequential circuit)
```



Rising edge or positive edge (posedge)  
Falling edge or negative edge (negedge)

x is recalculated as soon as  
c changes from 0 to 1 or  
d changes from 1 to 0.


## Synchronous triggers

```
always@ (posedge c or negedge d)
begin
    x=a +b;
end
```


storage unit

# Always Block (3/3)

```
module ALWAYS_BLOCK(IN , OUT);  
input [3 : 0]IN; output OUT; reg OUT;  
  
always @(IN)  
begin  
    OUT = (IN[0] | IN[1]) & (IN[2] | IN[3]);  
end  
endmodule
```

 
 
```
module D_FF(Clk, D, Q);  
input Clk, D;  
output Q;  
Reg Q;  
  
always @(posedge Clk)  
begin  
    Q=D;  
end  
endmodule
```



At every positive edge of signal Clk, Q is set as D.

# Variables

---

Nets:

```
wire a;      // 1-bit wire
wire [3:0] b; // 4-bit wire
```

## Three types of common variables in Verilog:

- (1) register (default width is 1 bit)
- (2) integer (default width is 32 bit)
- (3) parameter (default width is 1 bit)

```
reg a;      // 1-bit register
reg [3:0] b; // 4-bit register
integer c;   // single 32-bit
```

parameter [range] identifier=expression,  
identifier=expression,

integer

parameter d=4, e=6;  
Three variables (register, integer and parameter) are declared globally at the module level, or locally at the function level and begin-end block.

Verilog allows you to assign the value of a reg variable only within a function or an always block.

# Function

---

```
function [range] name_of_function;  
    function declaration  
    statement  
endfunction
```

1. Begin with function and end with endfunction
2. [Range] defines the width of the return value of the function (default is 1 bit)  
Contain one or more statements (enclosed inside a begin-end pair)
3. You can call function in a continuous assignment, always block or other functions

Function declaration:

**Input declaration:** specify the input signals for a function

**Output:** The output from a function is assigned to the function name.

Use concatenation operation to bundle several values for multi-outputs

# Function Statements (1/4)

Procedure assignments are assignment statements used inside a function.

(It is similar to C language, Note: it cannot be used in module)

They are similar to the continuous assignments, except that the left side of a procedural assignment can contain only reg and integer variables.

```
module FUN_STATE(A , B , C1 , C2 , C3 , C4 , C5);  
input [3 : 0]A; input [3 : 0]B;  
output [6 : 0]C1;           //0  
output [2 : 0]C2;           //discard  
output [4 : 0]C3;           //always  
output [4 : 0]C4;           //assign  
reg [6 : 0]C1; reg [2 : 0]C2;  
reg [4 : 0]C3; reg [4 : 0]C4;
```

```
function [4 : 0]Fn1;  
input [3 : 0]A; input [3 : 0]B;  
    Fn1 = A + B; // like C  
endfunction
```

```
always @(A or B)  
begin  
    C1 = Fn1(A , B);  
end  
always @(A or B)  
begin  
    C2 = Fn1(A , B);  
end
```

```
always @(A or B)  
begin  
    C3 = A + B;  
end
```

```
assign C4 = A + B;
```

```
endmodule
```

Three different ways to implement addition

# Function Statements (2/4)

```
input [3 : 0]A;      input [3 : 0]B;      // A and B are 4-bit
values
```

```
output [6 : 0]C1;    // C1 is 7-bit values
output [2 : 0]C2;    // C2 is 3-bit values
```


```
always @(A or B)
begin
```

```
    C1 = A + B;      // insert "0" in the first two bits
```

```
end
begin
```

```
    C2 = A + B ;    // discard the first two bits
```

```
end
```

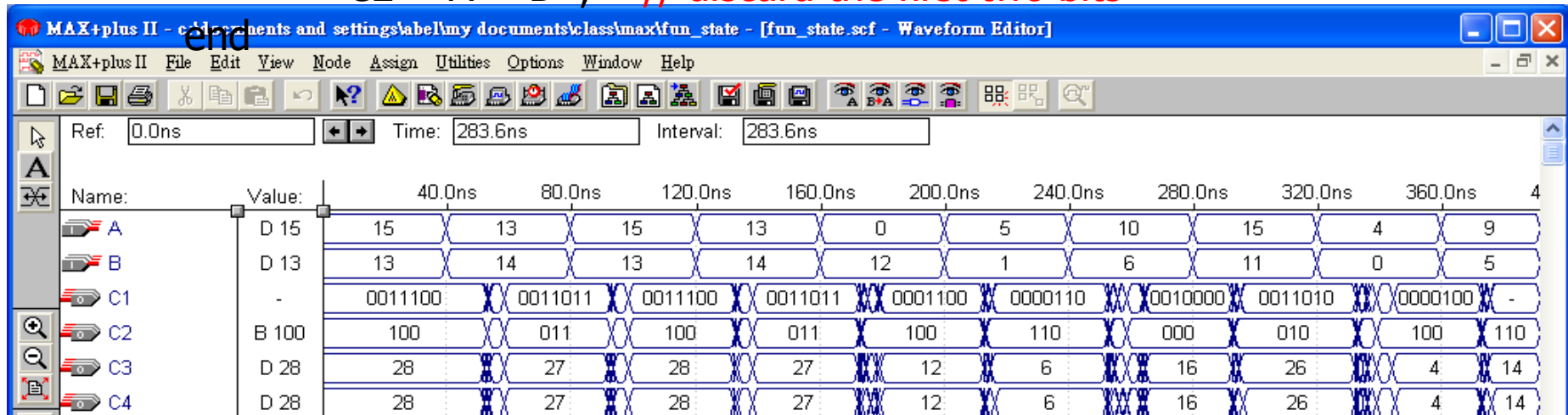



# Function Statements (3/4)


```
module test_n(a, b, x, y);  
input  a, b; output x, y;  
reg    x, y;  
function Fn1;  
    input a, b;  
    Fn1 = a & b;
```

*/\* begin-end is required  
for more statements \*/*

```
endfunction  
function Fn2;  
    input a, b;  
    Fn2 = a | b;  
endfunction  
always @(a or b)  
    begin  
        x = Fn1(a, b);  
        y = Fn2(a, b);  
    end  
endmodule
```

```
module test_n(a, b, x, y)  
input  a, b;  
output x, y;  
assign x=a & b;  
assign y=a | b;  
endmodule
```

```
module test_n(a, b, x, y);  
input  a, b;  
output x, y;  
reg    x, y;  
always @(a or b)  
begin  
    x = a & b;  
    y = a | b;  
end  
endmodule
```

 

## C language

```
x = a&b;  
y = a | b;
```

# Function Statements (4/4)

---

```
module test_n(a1, a, b, x, y);  
input [7:0] a1;  
input    a, b;  
output   x, y;  
reg      x, y;
```

```
function Fn1;  
input [width-1:0] a1;  
parameter width=8; //error message  
    input a, b;  
    Fn1 = a & b;  
endfunction
```

```
always @(a or b)  
    begin  
        x = Fn1(a1, a, b);  
    end  
endmodule
```

```
module test_n(a1, a, b, x, y);  
input [7:0] a1;  
input    a, b;  
output   x, y;  
reg      x, y;
```

```
function Fn1;  
parameter width=8;  
input [width-1:0] a1; // OK  
    input a, b;  
    Fn1 = a & b;  
endfunction
```

```
always @(a or b)  
    begin  
        x = Fn1(a1, a, b);  
    end  
endmodule
```

Can we input width with scanf or  
input ??  
why?

# Example-Function

```
module FUN_ALL(A , B , Y1 , Y2);
input [3 : 0] A,B;output [4 : 0] Y1, Y2;
reg [4 : 0] Y1, Y2;
```

```
function [4 : 0] Fn2;
input [3 : 0] F1 , F2;
begin
    Fn2 = F1 + F2;
end
endfunction
```

```
function [4 : 0] Fn1;
input [3 : 0]F1 , F2;
begin
    Fn1 = Fn2(F1 , F2) + 2;
end
endfunction
```

```
always @(A or B)
begin
    Y1 = Fn1(A , B);
    Y2 = Fn2(A , B);
end
endmodule
```

$Y1 = A + B + 2$   
 $Y2 = A + B$

